

ASSIGNMENT - 07

Name : Mosraor Mofiz Arman

ID : 1921079642

Course : CSE231

Section : 10.

Submitted to : Dr. Mohammad Moniruzzaman Khan


Date : 05-04-2021.

I

The universal property of NAND and NOR gates.

Truth table for 2 input NAND gate.

(a)

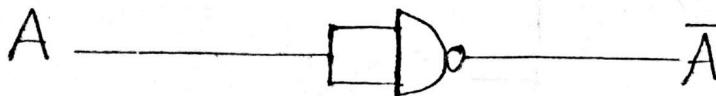

A	B	X
0	0	1
0	1	1
1	0	1
1	1	0

fig: A NAND gate used as an inverter.

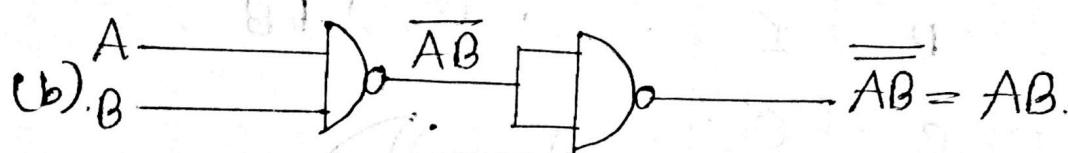


fig: Two NAND gates used as an AND gate.

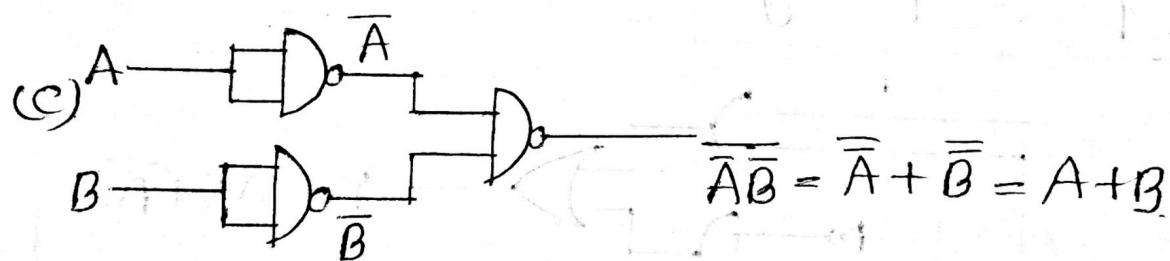


fig: Three NAND gates used as an OR gate.

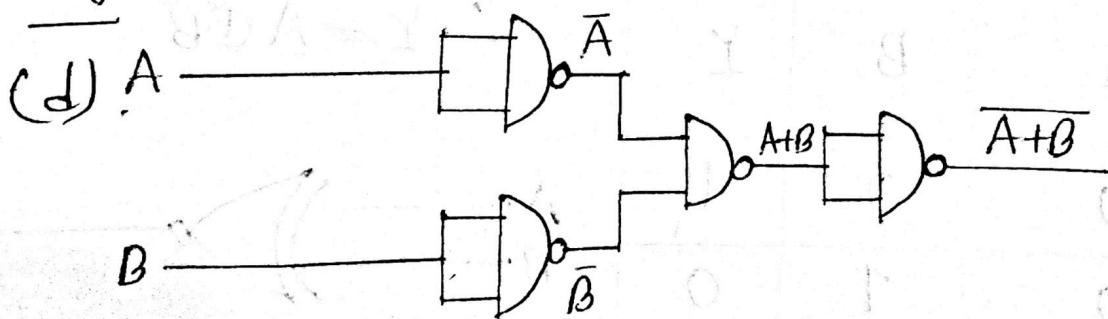



fig: Four NAND gates used as NOR gate.

The NOR Gate as a universal logic element.

Truth table for 2 input NOR Gate.



Fig: a NOR gate used as an inverter.

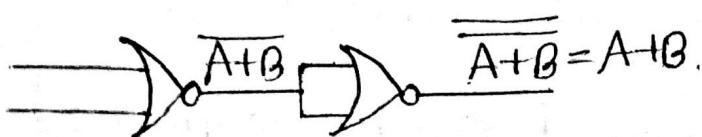

A	B	X
0	0	1
0	1	0
1	0	0
1	1	0

Fig: Two NOR gates used as an OR gate.

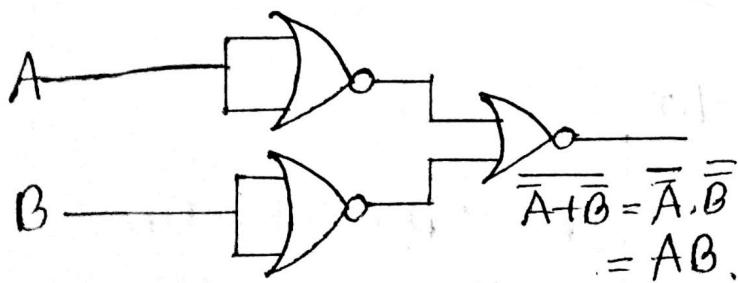


Fig: Three NOR gates used as an AND gate.

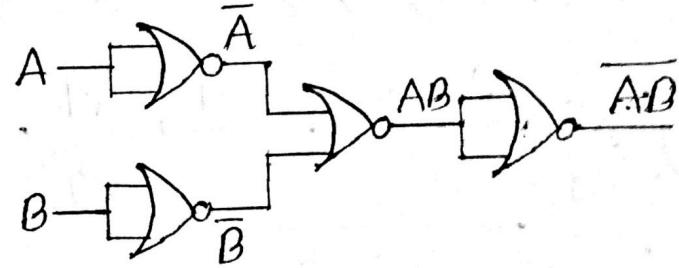


Fig: Four NOR gates used as a NAND gate

Simplify the Boolean Function in :

- (a) Sum of products form
- (b) Product of sum form.

$$F(A, B, C, D) = \sum(0, 1, 2, 5, 8, 9, 10)$$

(a) $AB \backslash CD$

		D		00		01		11		10	
		0	1	0	1	3	2	1	0	2	1
B		00	(1)	01	(1)	11		10		10	
		11		11	(1)	13		15		14	
A		11		11	(1)	13	(1)	15		14	
		10	(1)	10	(1)	11		11	(1)	10	

$F = \overline{BC} + \overline{BD} + \overline{ACD}$

In product of minterms, F can be expressed as

$$F(A, B, C, D) = \prod (3, 4, 6, 7, 11, 12, 13, 14, 15)$$

(b) $AB \backslash CD$

		D		00		01		11		10	
		0	1	00	01	01	10	11	10	10	10
B		00						(0)			
		01	(0)					0			
A		01	(0)					0			
		11	(0)	(0)		0	0	0	(0)		
C		11	(0)	(0)		0	0	0	(0)		
		10						(0)			

$F = \overline{CD} + AB + BD$

$F = \overline{CD} + AB + BD$

$= (\overline{CD}). (AB). (BD)$

$= (\overline{C} + \overline{D}) (A + B) (B + D)$

Combinational Logic using NAND and NOR gates:

NAND gate:

using De Morgan's rule :

$$\overline{AB} = \overbrace{\overline{A} + \overline{B}}$$

Negative OR.


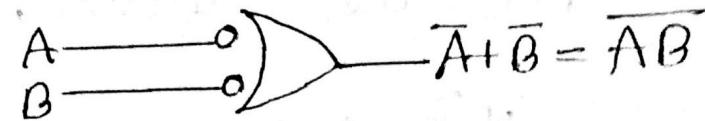
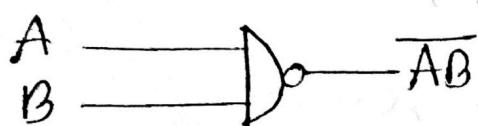


Fig : Two graphic symbols for NAND gate.

$$\overline{A+B} + \overline{AB}$$

Negative AND.

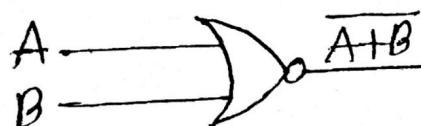

OR-invert.

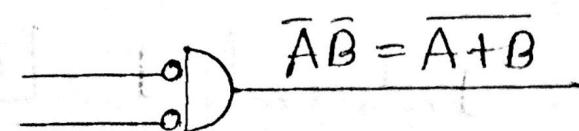


Fig : Two graphic symbols for NOR gate.

Assignment : 07 (Questions)

(1) $A + \overline{B}C$

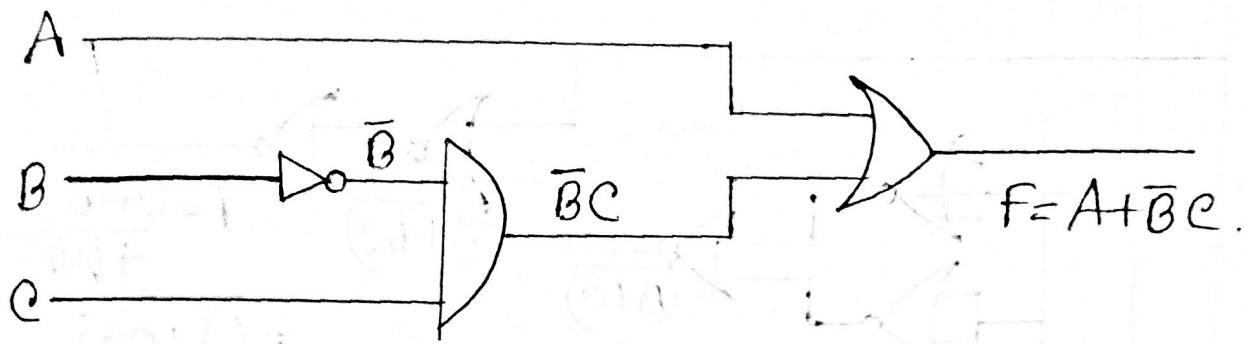


Fig : Normal Logic circuit.

(2) $A + \overline{B}C$

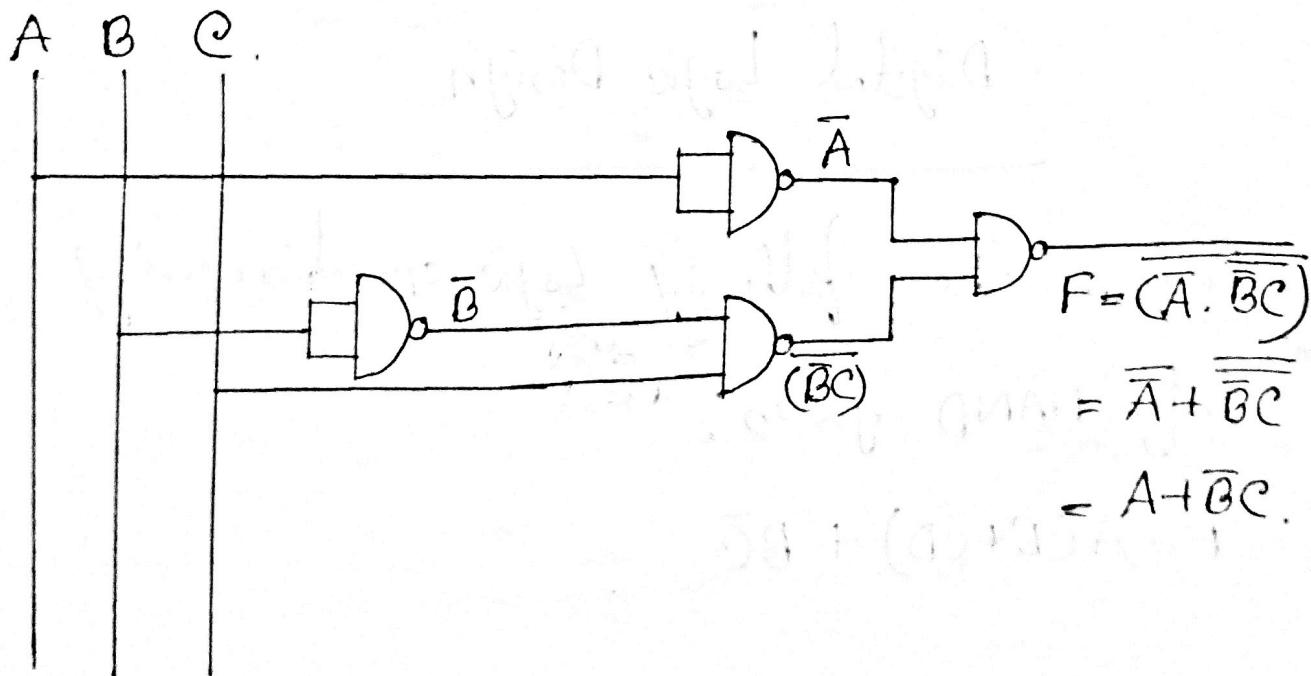


Fig : Logic circuit using NAND gate (universal gate).

$$(3) A + \bar{B}C.$$

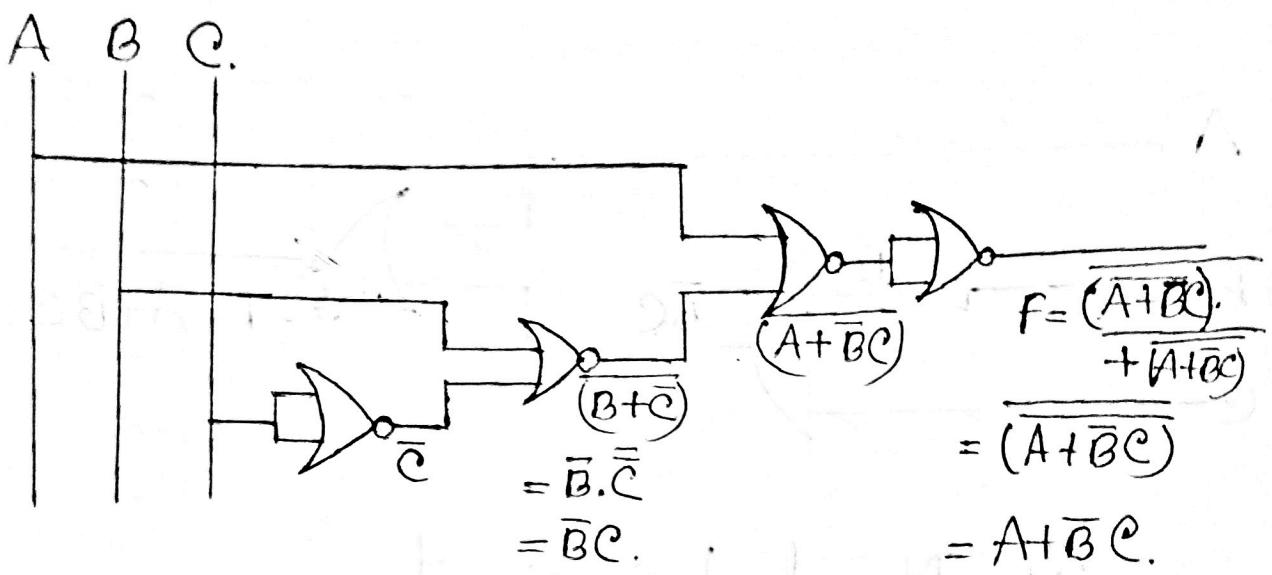


fig: Logic circuit using NOR gate (Universal gate)

Digital Logic Design

Perform the following logic operation using only NAND gates:

$$F = A(B+CD) + B\bar{C}$$

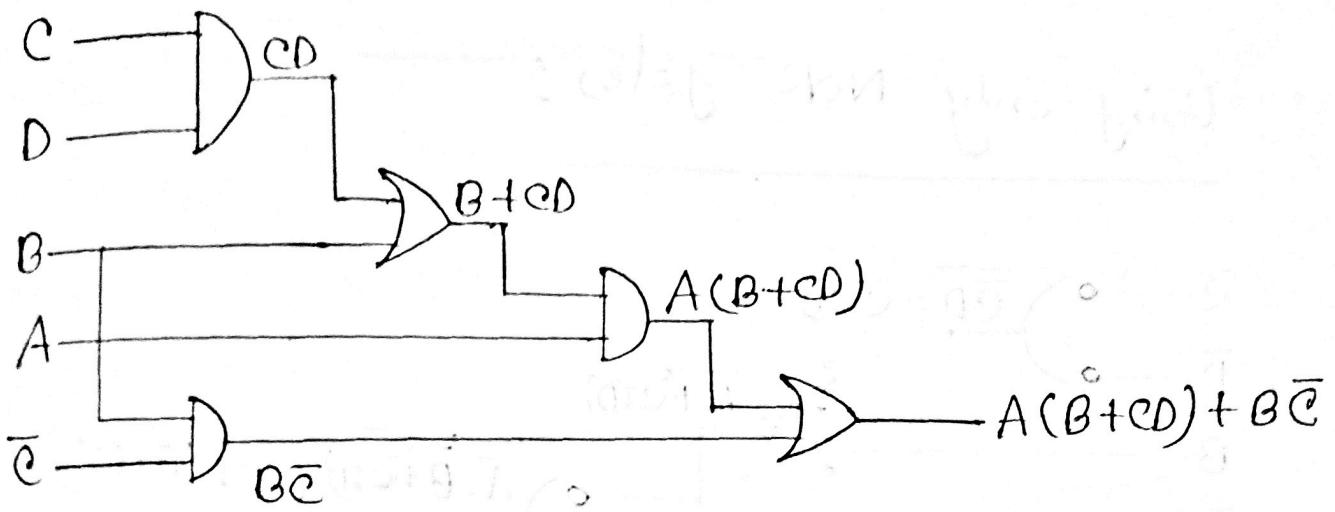


Fig: AND/OR implementation.



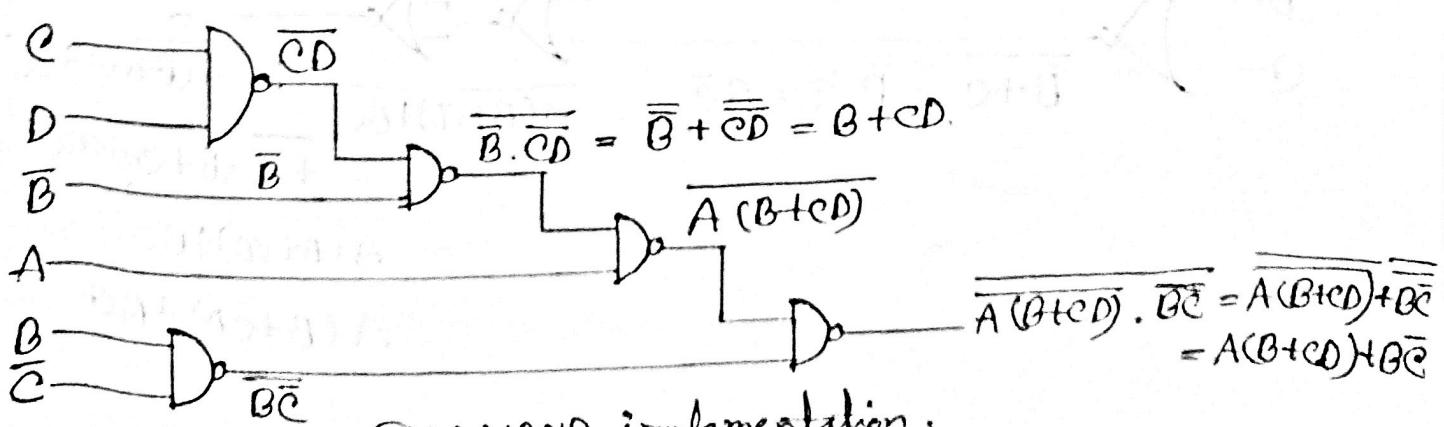
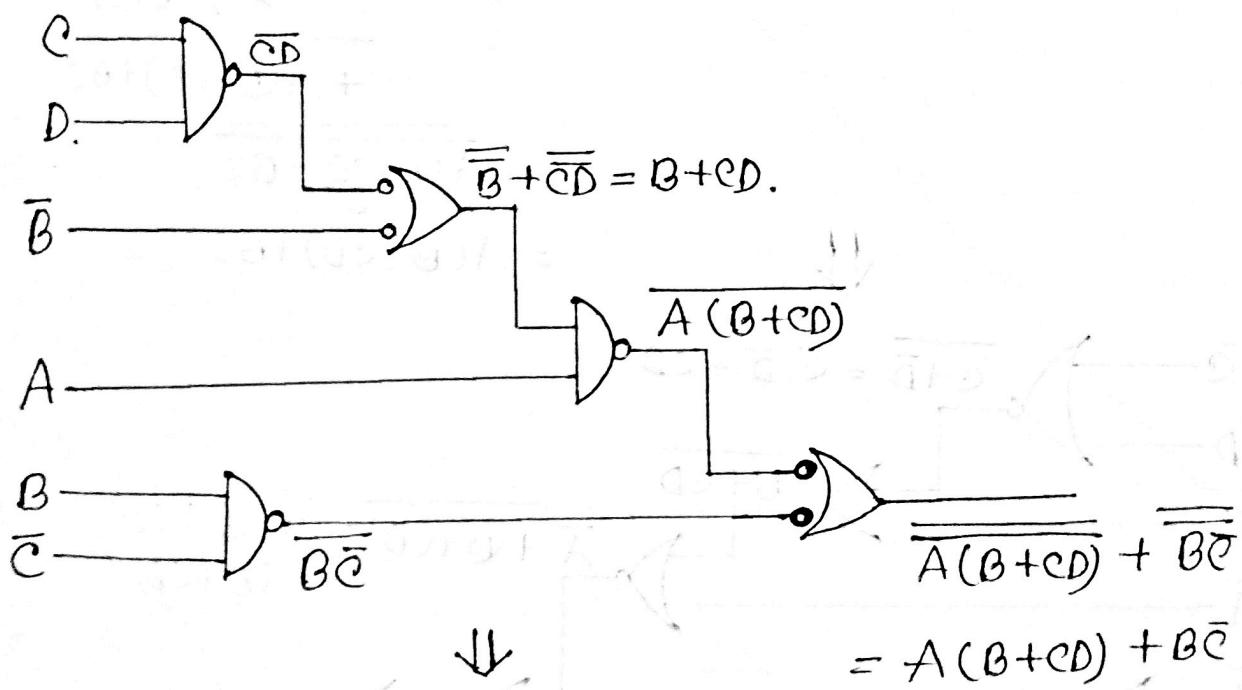
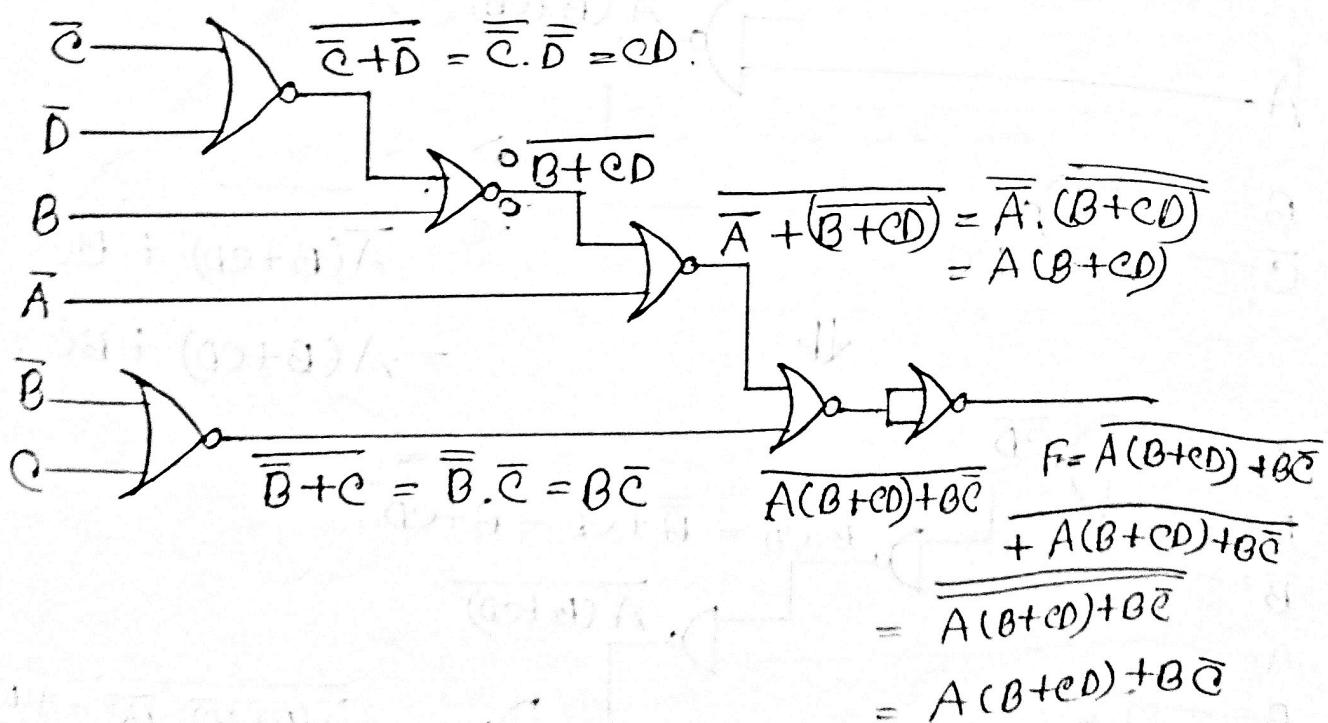


Fig: NAND implementation.

Using only NOR gates:

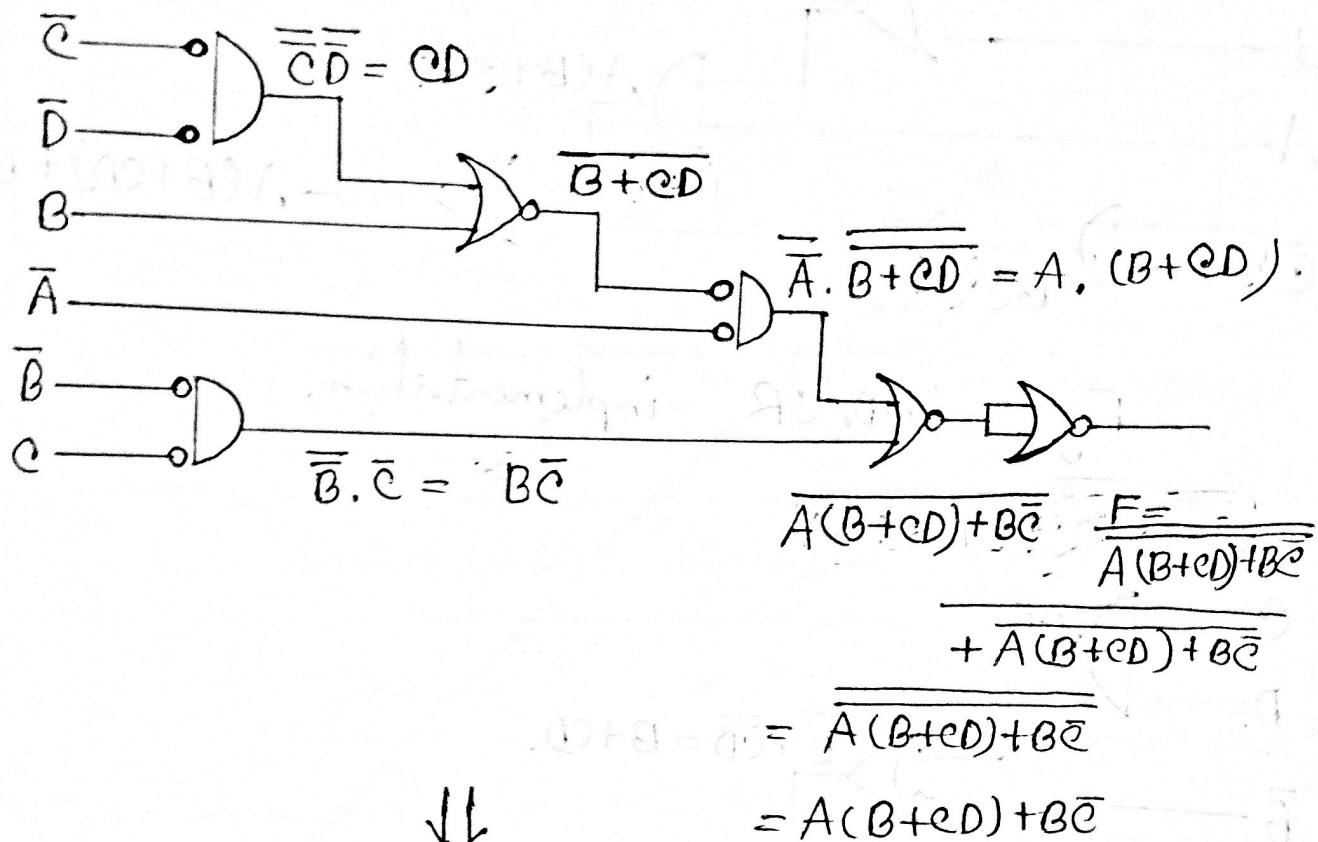

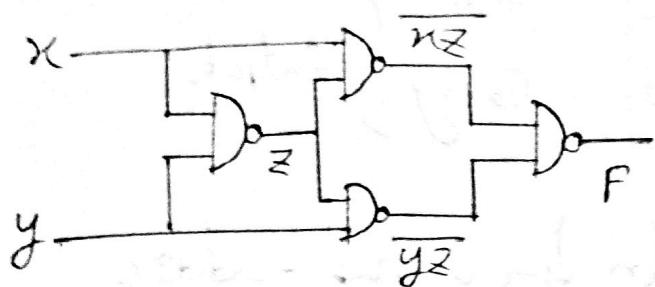Determine the truth table for the following :



x	y	$z = \bar{y}z$	$\bar{x}z$	$\bar{y}z$	F
0	0	1	1	1	0
0	1	1	1	0	1
1	0	1	0	1	1
1	1	0	1	1	0

$$\therefore F = x \oplus y$$

The Half Adder :

Basic rules for binary addition :

$$0+0=0$$

$$0+1=1$$

$$1+0=1$$

$$1+1=10.$$

These operations are performed by a logic circuit called a half-adder.

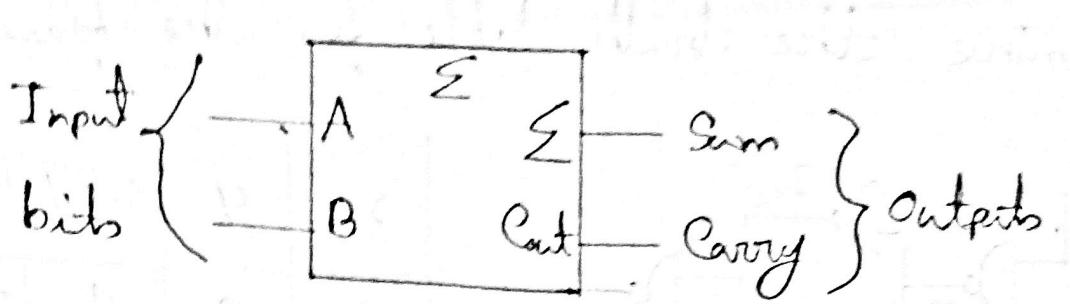


Fig : Block Diagram for a half-adder.

Half-adder truth table:

A	B	Cout	Σ
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

The sum bit can be expressed as

$$\Sigma = A \oplus B$$

The carry bit can be expressed as

$$C_{out} = AB$$

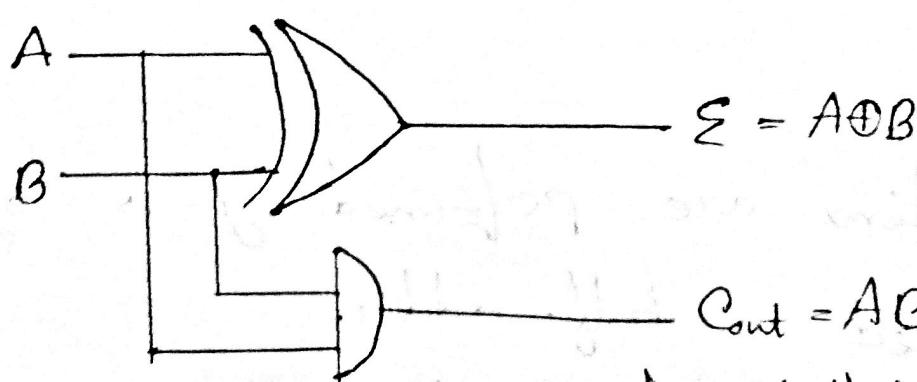


Fig : Logic Diagram for a half-adder.

The Full Adder :

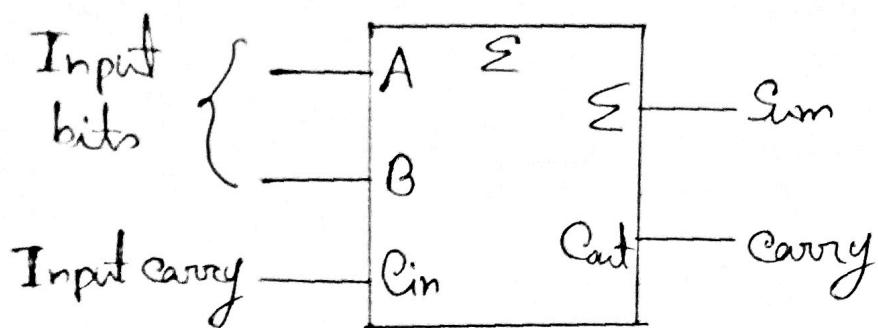


Fig : Block Diagram for a full-adder.

Full-adder truth table :

A	B	Cin	Cout	Σ
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

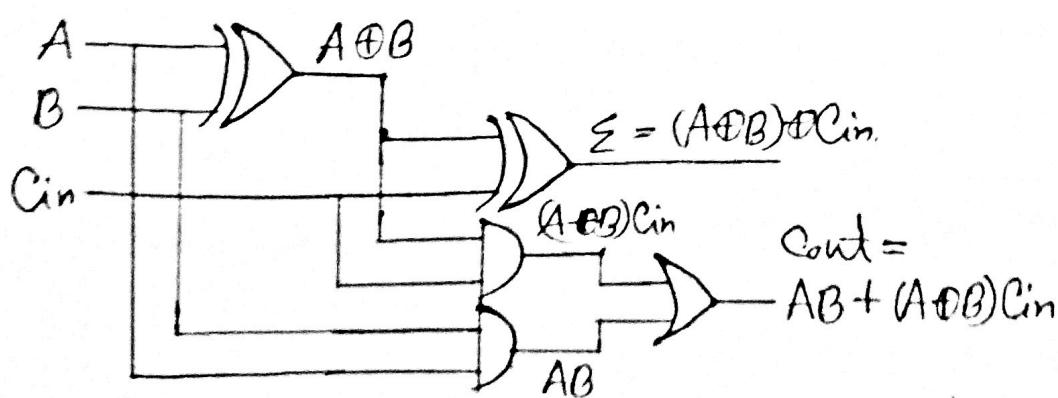


Fig : Complete logic circuit for a full adder.