

CSE231
SEC: 06

Project

Seven-Segment Display Using Sequential Circuit
on
BABAFABA

Submitted to:

Dr Mohammad Monirujjaman Khan

Group Members:

1. Kazi Mahbub Jamil 1921626042
2. Mahinur Sazib Sristy 192105504
3. Md. Sihab Bhuiyan 1912403642
4. Md. Adib Sadman 1921050042

Written By :
Kazi Mahbub Jamil

Date:

22 Jan,2021

Table of Content:

1. Introduction
2. Encoder & Decoder
3. Seven-Segment Display
4. About 555 Timer
5. How 555 Timer Works
6. Asynchronous & Synchronous circuit
7. Reason behind choosing Asynchronous circuit
8. Truth Table
9. Derived Equation using SOP
10. K-map & Circuit Diagram
11. Sequential circuit
12. Logisim
13. Conclusion

Introduction:-

In this project we are going to see definition and implementation of encoder, decoder, seven-segment display. By all this we can learn how to display many thing to seven-segment display. We will also know the simplification by using K-map.

The given project is to portray "BABAFABA" to the seven-segment display with its truth table, simplified circuit and also the simplification of K-map and it's circuit.

Encoder:-

By encoder in digital logic means a combinational circuit that converts binary information in the form of a 2^n input lines into n output lines, which represent n -bit code for the input. The purpose of encoder is standardization, speed, secrecy, security or saving space by shrinking size.

Decoder:-

A combinational circuit that converts n lines of input into 2^n lines of output, which means decoder represent the opposite of encoder. A decoder can take the form of a multiple-input, multiple-output logic circuit that converts coded input into coded output, where the input and output codes

are different. Decoding is necessary
in application such as data multiple
-xing, 7 segment display and memory
address decoding.

Seven-Segment Display :-

We know, A seven-segment display is a set of seven bar shaped LCD elements, which are arranged to form a squared-off figure 8. Seven-segment displays use other illumination devices, such as - incandescent or gas-plasma lamps. If all elements are activated, the display shows a numeral 8. When some of the elements are activated but not others, any single-digit numeral from 0 to 9, as well as most uppercase and lowercase letters of the English can be portrayed.

About 555 timer:-

The 555 is a single-chip version of a commonly used circuit called a multivibrator, which is useful in a wide variety of electronic circuits. The 555 timer chip probably the most popular integrated circuit ever made.

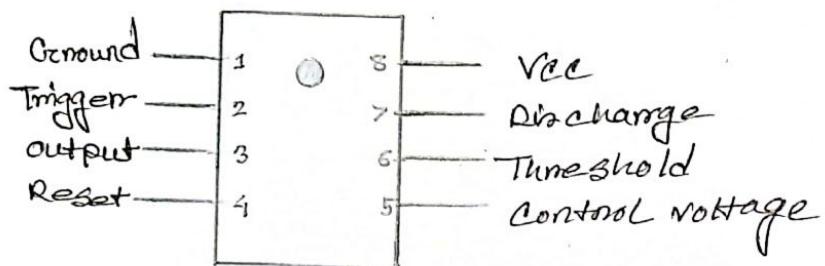


Figure: A 555-timer chip

The 555-timer is a highly stable device for generating accurate time delays or oscillation. Additional terminals are provided for triggering or resetting if desired. In the time delay mode of operation, the timer is precisely controlled by one external resistor and capacitor.

555

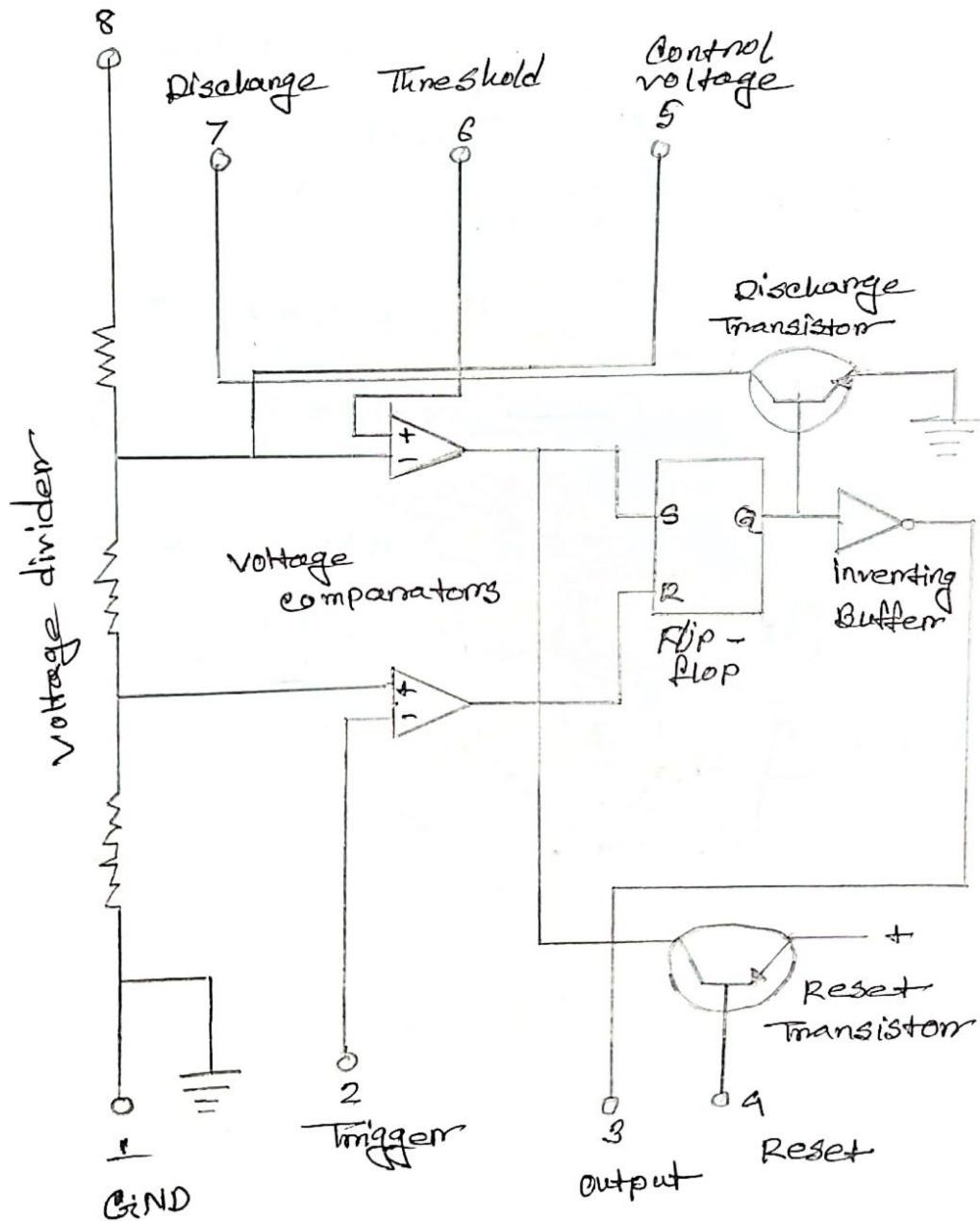


Figure: Internal Construction Of 555 Timer

How all 8 pins are working:-

Pin 1 : In The grounded terminal all the voltages are measured with respect to this terminal.

Pin 2 : Trigger terminal is an inverting input to a comparator that is responsible for transition of flip-flop from set to reset. The output of the timer depends on the amplitude of the external trigger pulse applied to this pin.

Pin 3 : Output of the timer is available at this pin. There are two ways in which a load can be connected to the output terminal either between pin 3 and ground pin(1) or between pin 3 and supply pin(8).

Pin-4 : (Reset terminal) - To disable or reset the timer a negative pulse is applied to this pin due to the fact it is referred to as reset terminal. When this pin is not to be used for reset purpose, it should be connected to +V_{cc} to avoid any possibility of false triggering.

Pin-5 : (Control voltage) - The function of this terminal is to control the threshold and trigger levels. Thus either the external voltage or a pot connected to this pin determines the pulse width of the output waveform.

Pin-6 : Threshold terminal is the non-inverting input terminal or comparator 1, which compares the voltage applied to the terminal with a reference voltage of $\frac{2}{3} V_{cc}$. The amplitude

of voltage applied to this terminal is responsible for the set state of flip flop.

Pin-7 : Discharge Terminal is connected internally to the collector of transistor and mostly a capacitor is connected between this terminal and ground. It is called discharge terminal because when transistor saturates, capacitor discharge through the transistor.

Pin-8 : It is a supply terminal. A supply voltage of +5V to +18 V is applied to this terminal with respect to the ground. (Pin 1)

Asynchronous & Synchronous circuit:-

Sequential circuit is one of the major categories of digital logic circuits. Based on the clock input, it is further classified into synchronous and asynchronous circuits.

Synchronous sequential circuit : This circuits are digital circuits governed by clock signals. The transition from one state to another state takes place only by the application of specified clock signals, even if the input changes. Clocked flip-flops are used as memory elements in synchronous sequential circuits. The state of synchronous sequential circuits are always predictable and thus reliable. Also it is easy to design synchronous sequential circuits.

But synchronous sequential circuits are slower in its operation speed. This is due to the propagation delay of clock signal in reaching all elements of the circuit. The distributed clock signal consumes large power and dissipates large amount of heat.

Asynchronous Sequential circuit: These circuits are digital circuits that are not driven by clock. They can be called as self-timed circuit. The transition from one state to another takes places immediately once the inputs change. There are chances for the asynchronous circuit to enter into a wrong state because of the time difference between the arrivals of inputs. It is hard to make a asynchronous circuit but it is less power-hungry than synchronous and


also they are comparatively faster than synchronous circuits.

For,

All of these reasons we are going to build our sequential circuit using the asynchronous circuit.

Our project on BA BA FA FA

Let's point it,

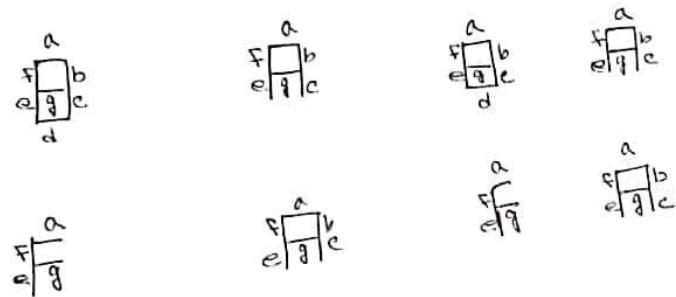

Truth Table

x	y	z	a	b	c	d	e	f	g	word
0	0	0	1	1	1	1	1	1	1	日
0	0	1	1	1	1	0	1	1	1	F
0	1	0	1	1	1	1	1	1	1	日
0	1	1	1	1	1	0	1	1	1	F
1	0	0	1	0	0	0	1	1	1	F
1	0	1	1	1	1	0	1	1	1	F
1	1	0	1	0	0	0	1	1	1	F
1	1	1	1	1	1	0	1	1	1	F

Figure: Table 1

Derive equation using sum of
Product:

$$a = \bar{x}\bar{y}\bar{z} + \bar{x}\bar{y}z + \bar{x}yz + \bar{x}yz + xy\bar{z} + xy\bar{z}$$
$$+ xyz + xyz$$

$$b = \bar{x}\bar{y}\bar{z} + \bar{x}\bar{y}z + \bar{x}yz + \bar{x}yz + xy\bar{z} + xyz$$

$$c = \bar{x}\bar{y}\bar{z} + \bar{x}\bar{y}z + \bar{x}yz + \bar{x}yz + xy\bar{z} + xyz$$

$$d = \bar{x}\bar{y}\bar{z} + \bar{x}\bar{y}z$$

$$e = \bar{x}\bar{y}\bar{z} + \bar{x}\bar{y}z + \bar{x}yz + \bar{x}yz + xy\bar{z} +$$

$$xy\bar{z} + xyz + xyz$$

$$f = \bar{x}\bar{y}\bar{z} + \bar{x}\bar{y}z + \bar{x}yz + \bar{x}yz + xy\bar{z} +$$

$$xy\bar{z} + xyz + xyz$$

$$f = \overline{x}\overline{y}\overline{z} + \overline{x}\overline{y}z + \overline{x}yz + \overline{x}y\overline{z} + xy\overline{z} + xyz + xy\overline{z} + x\overline{y}z$$


It's look's by using sop the equation
is too much large for simplifying. So,
make that a small equation; now
we are using k-map..

K-map for A :

x	00	01	11	10
0	1	1	1	0
1	1	1	1	1

$$F = x + \bar{x} = 1$$

Circuit Diagram of A :

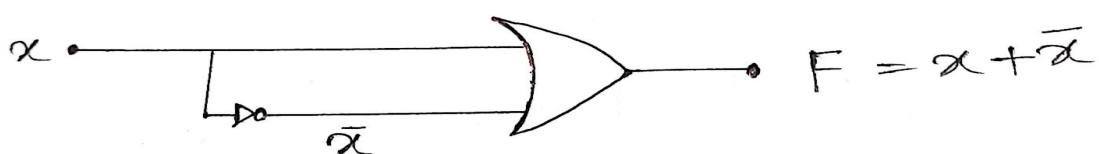


K-map for B :

		yz	xz	xz	xz
		00	01	11	10
0		1	1	1	1
1	0	1	0	0	1

$$\begin{aligned}F &= \bar{x} + \bar{y}\bar{z} + y\bar{z} \\&= \bar{x} + \bar{z} (y + \bar{y}) \\&= \bar{x} + \bar{z}\end{aligned}$$

Circuit Diagram of B :

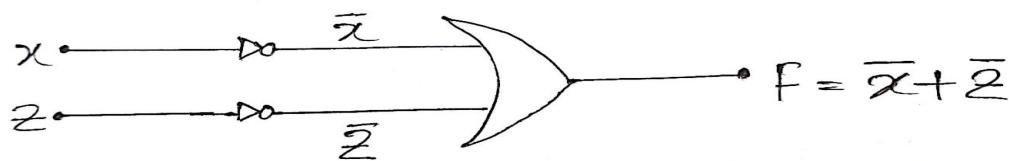

K-map for C:


x/z	00	01	11	10
0	1	1	1	0
1	1	0	0	1

$$f = \bar{x} + \bar{y}\bar{z} + y\bar{z}$$

$$= \bar{x} + \bar{z}(y + \bar{y})$$

$$= \bar{x} + \bar{z}$$

Circuit Diagram of C:

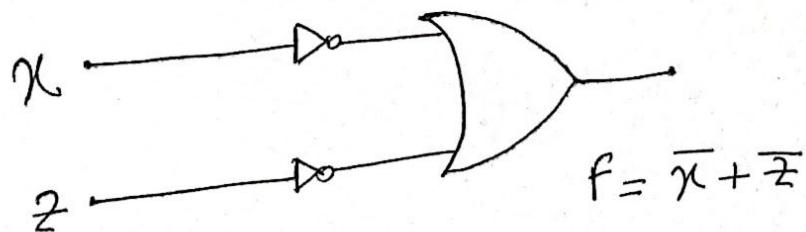

K-map for d :

		z\y	00	01	11	10
		x	0	1	1	0
		0	1	0	1	0
		1	0	0	0	0

$$\begin{aligned} F &= \bar{x}\bar{y}\bar{z} + \bar{x}yz \\ &= \bar{x}(\bar{y} + \bar{z} + yz) \\ &= \bar{x} \end{aligned}$$

Circuit Diagram of D :

$$x \rightarrow D \rightarrow \bar{x} \rightarrow F = \bar{x}$$


K-map for E:

	x_2	x_1	y_2	y_1
x_1	00	01	11	10
0	1	1	1	1
1	1	1	1	1


$$F = x + \bar{x}$$

$$= 1.$$

Circuit Diagram of E:

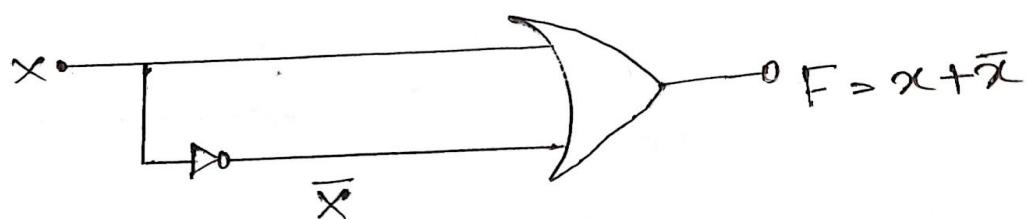


K-map for f :

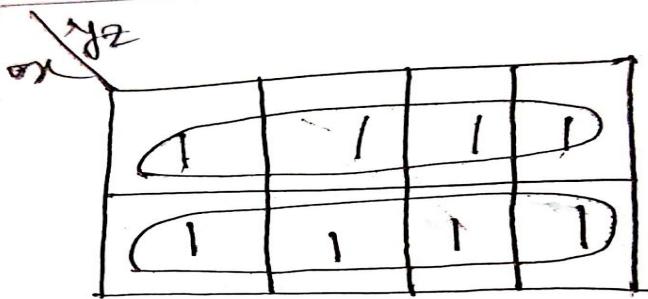


$$\begin{aligned} F &= \bar{x} + \bar{x} \\ &= 1 \end{aligned}$$

Circuit Diagram of F :

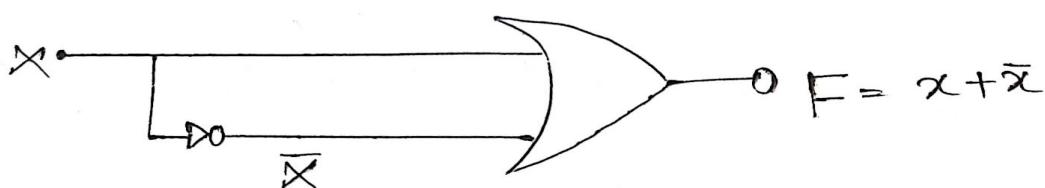

K-map for $f = x + \bar{x}$

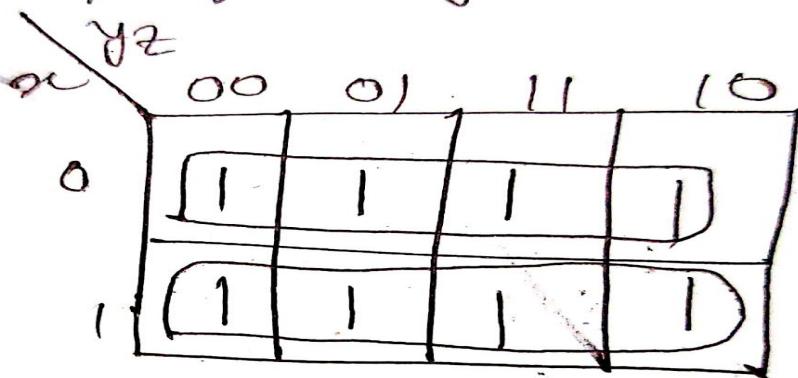

$$\begin{aligned} F &= x + \bar{x} \\ &= 1 \end{aligned}$$

Circuit Diagram of G :

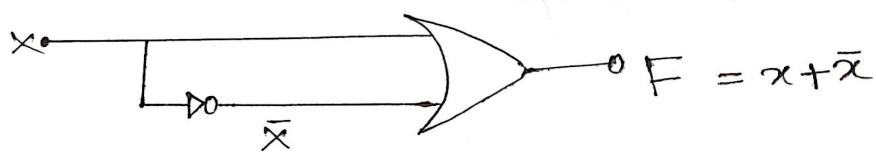


Table :

clock pulse	Q ₂	Q ₁	Q ₀	Display	a	b	c	d	e	f	g
Initially	0	0	0	000	1	1	1	1	1	1	1
1	0	0	1	011	1	1	1	0	1	1	1
2	0	1	0	001	1	1	1	1	1	1	1
3	0	1	1	010	1	1	1	0	1	1	1
4	1	0	0	F	1	0	0	0	1	1	1
5	1	0	1	011	1	1	1	0	1	1	1
6	1	1	0	F	1	0	0	0	1	1	1
7	1	1	1	010	1	1	1	0	1	1	1
8	0	0	0	x	x	x	x	x	x	x	x

Figure: Table 2

$$B \rightarrow \bar{Q}_0 \bar{Q}_1 \bar{Q}_2$$

$$A \rightarrow \bar{Q}_0 \bar{Q}_1 Q_2$$

$$B \rightarrow \bar{Q}_0 Q_1 \bar{Q}_2$$

$$A \rightarrow \bar{Q}_0 Q_1 Q_2$$

$$F \rightarrow Q_0 \bar{Q}_1 \bar{Q}_2$$

$$A \rightarrow Q_0 \bar{Q}_1 Q_2$$

$$F \rightarrow Q_0 Q_1 \bar{Q}_2$$

$$A \rightarrow Q_0 Q_1 Q_2$$

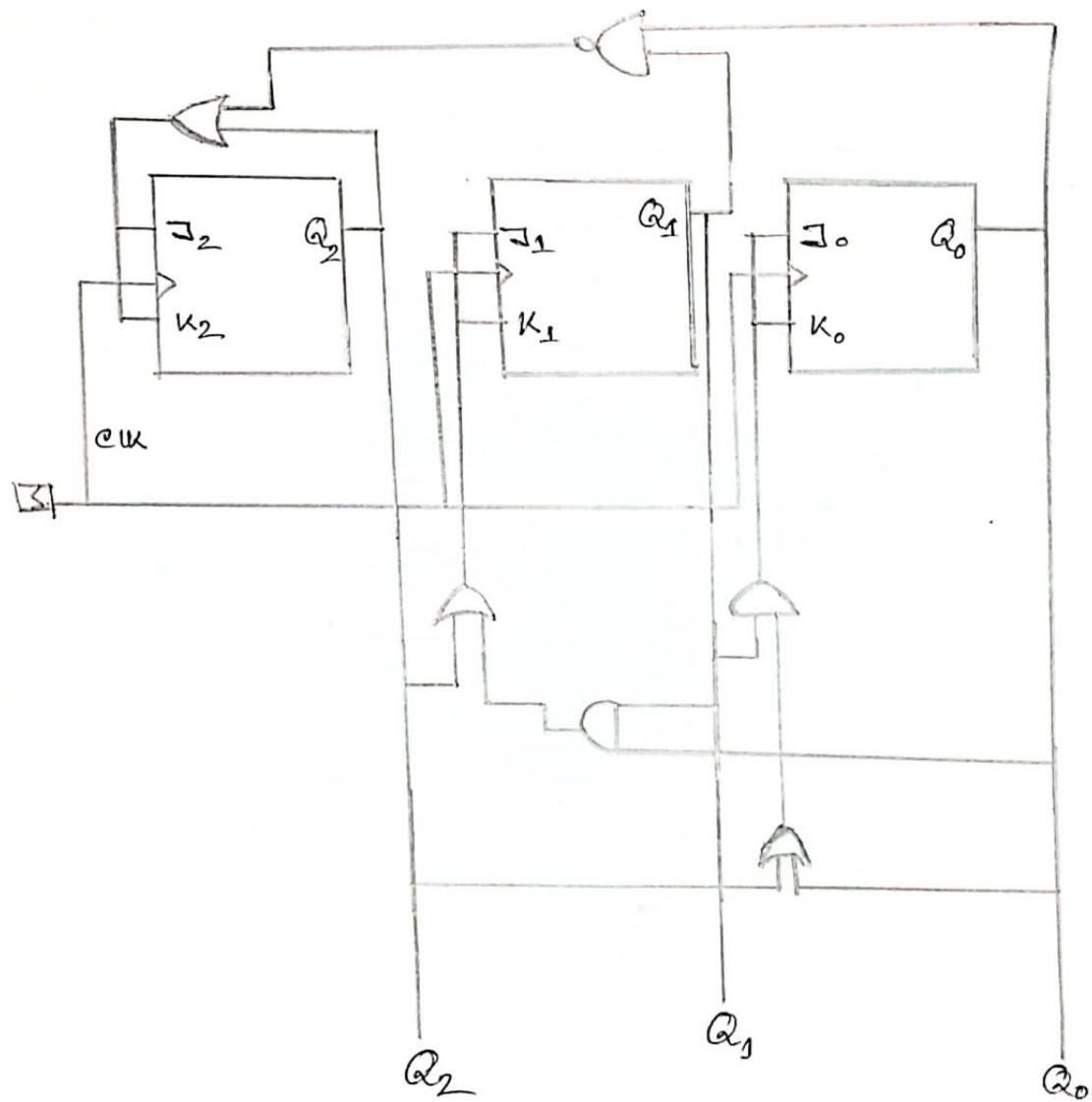


Figure: Sequential circuit Diagram

Logisim

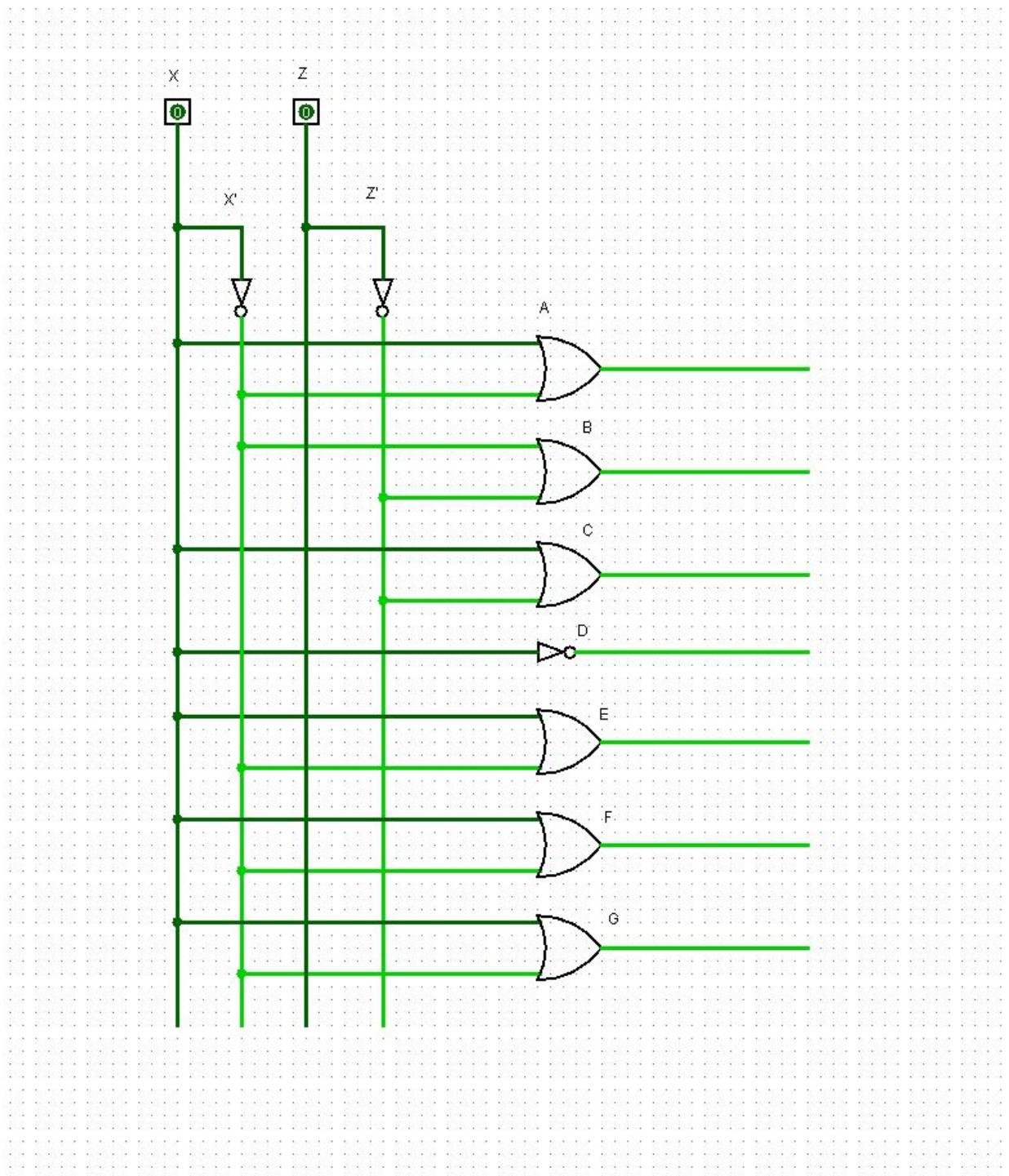


Figure A.1: Circuit on logisim form k map

Logisim without sequential circuit: On BABAFAFA

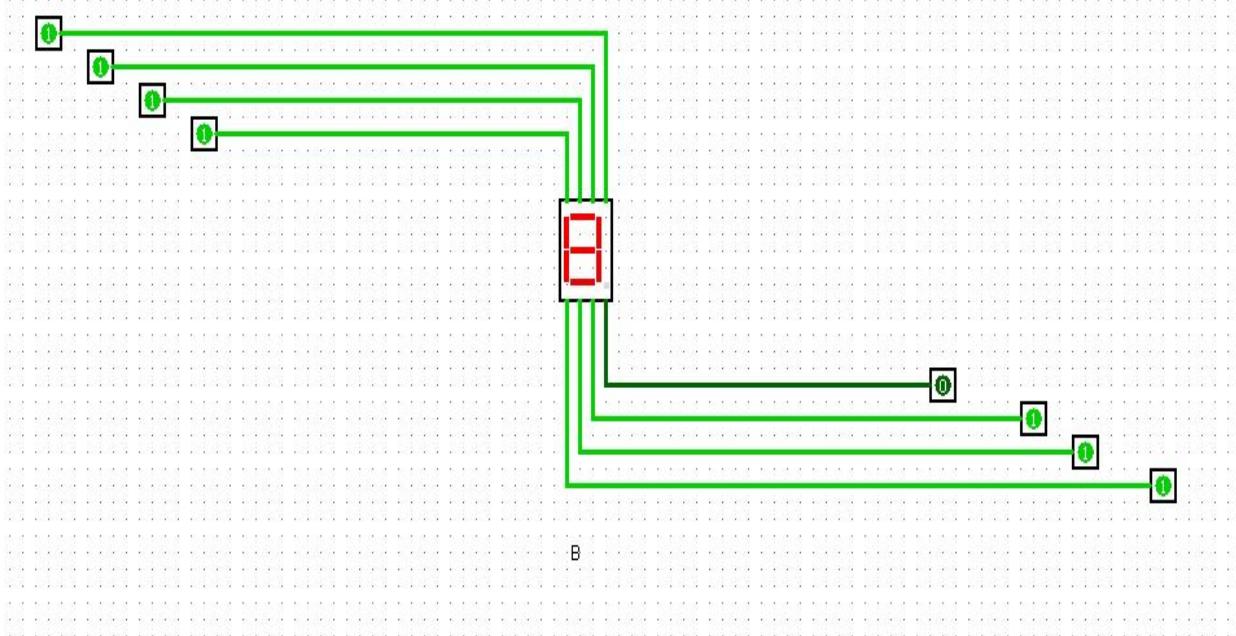


Figure B.1:B

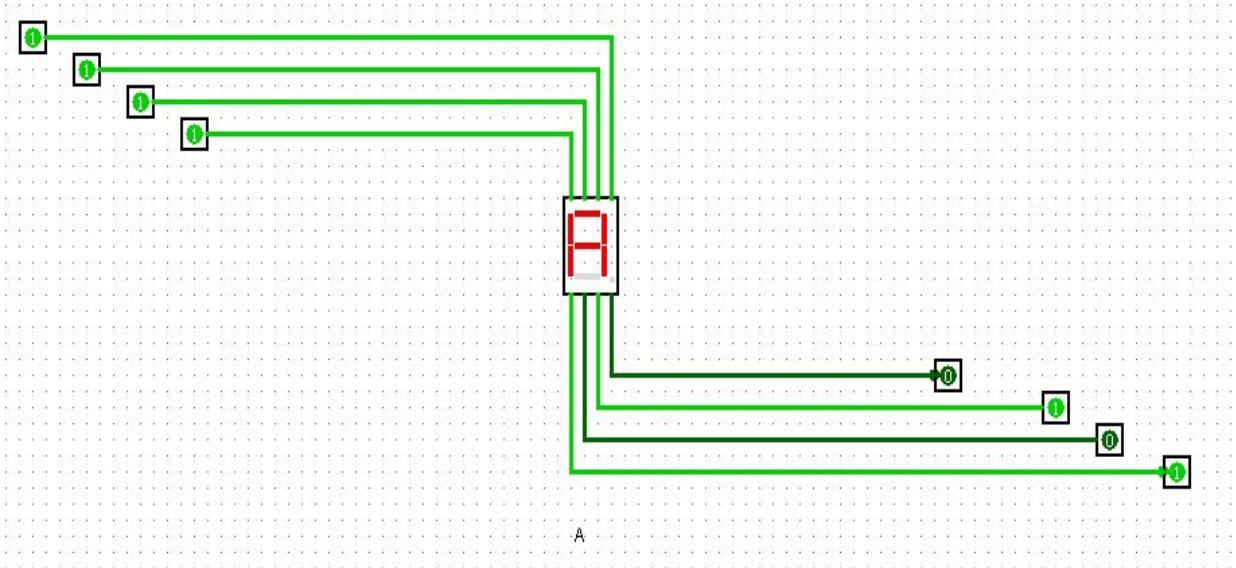


Figure B.2: A

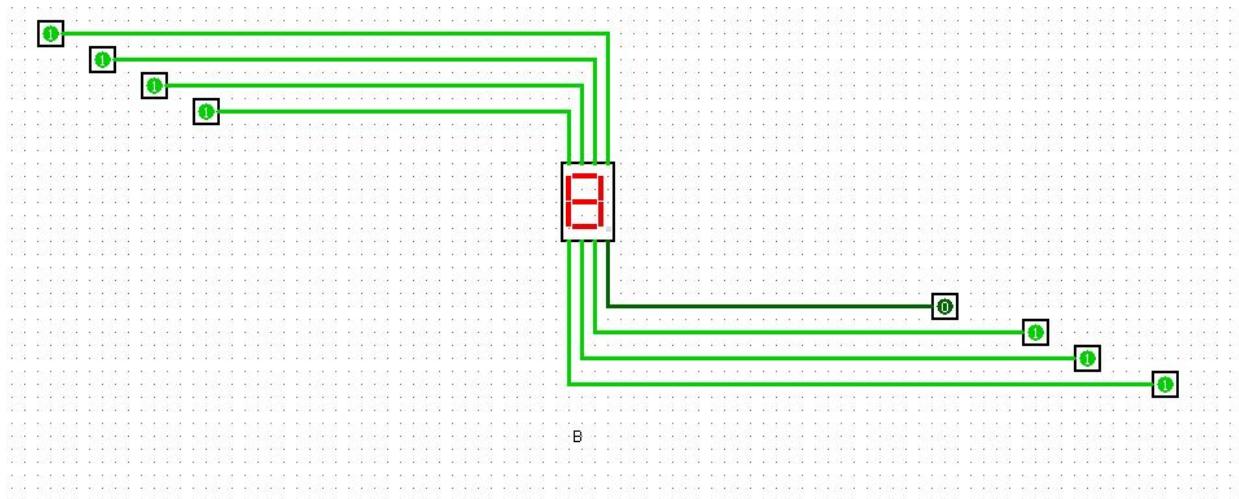


Figure B.3 : B


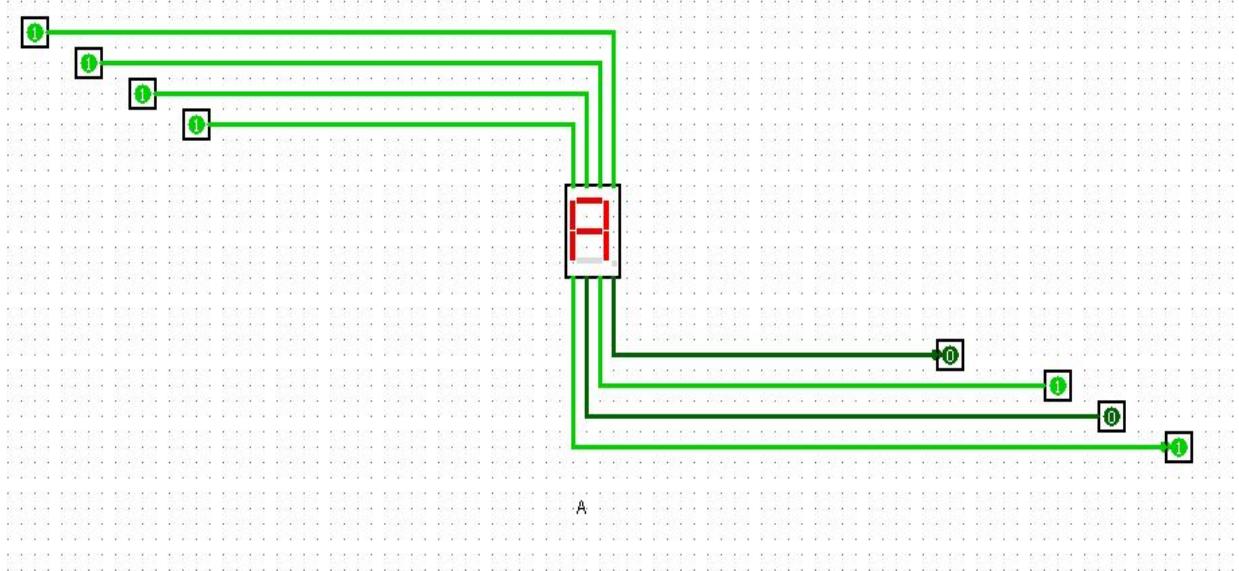
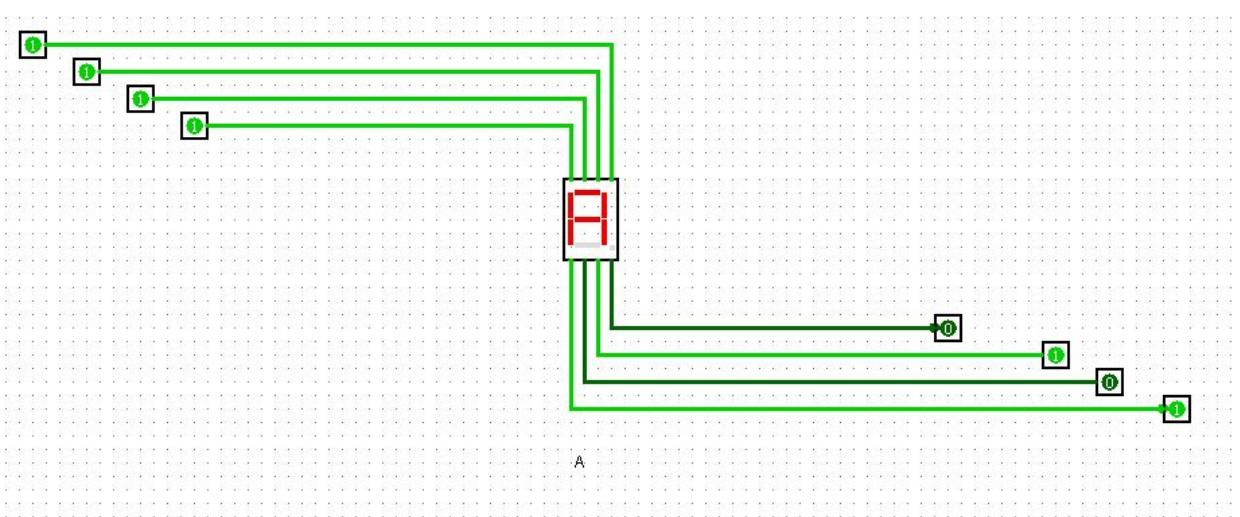


Figure B.4: A

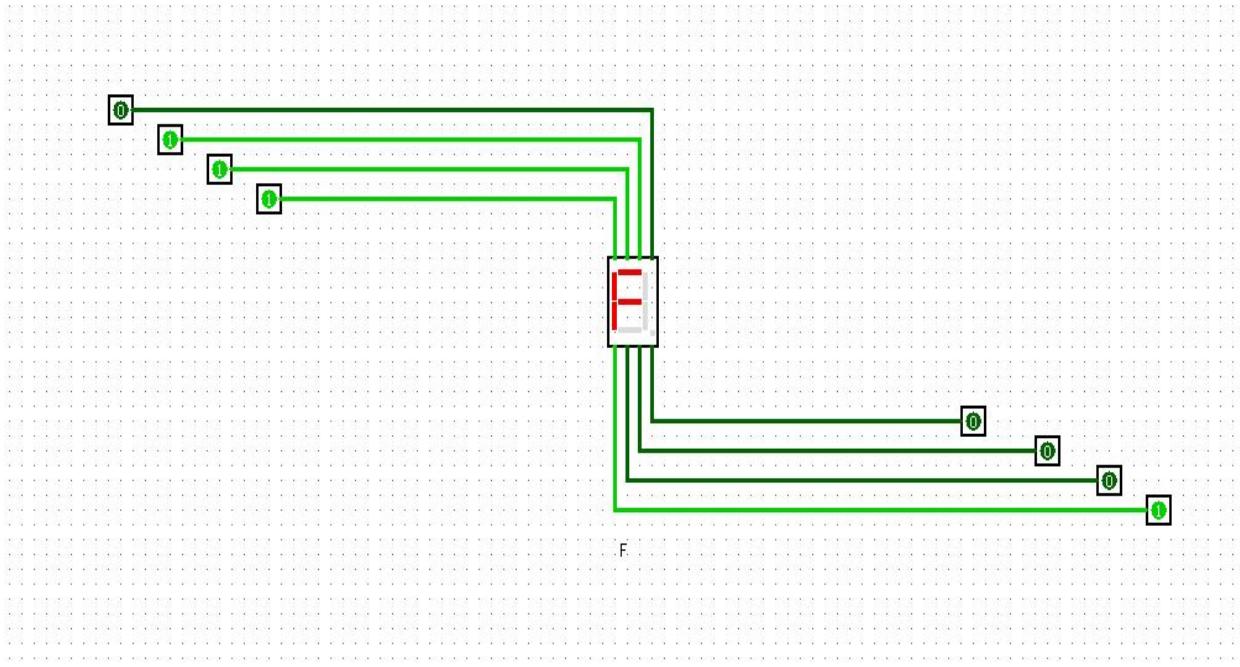

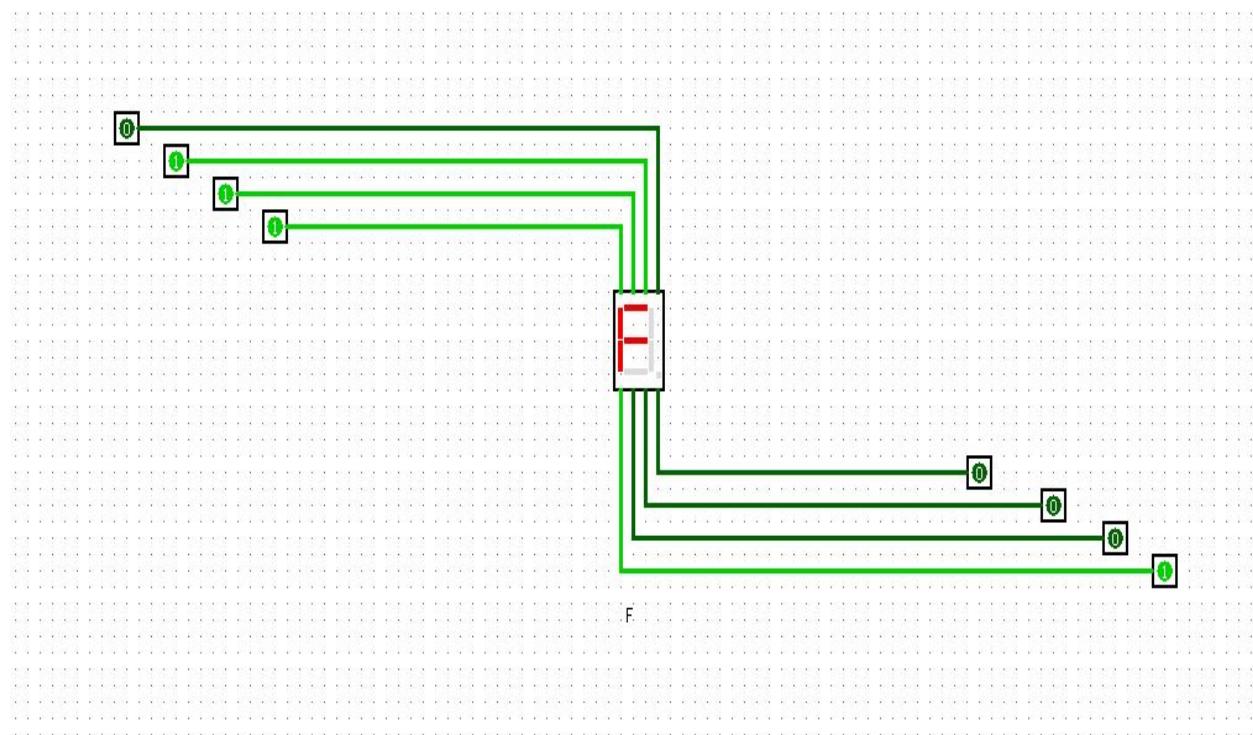


Figure B.7: F

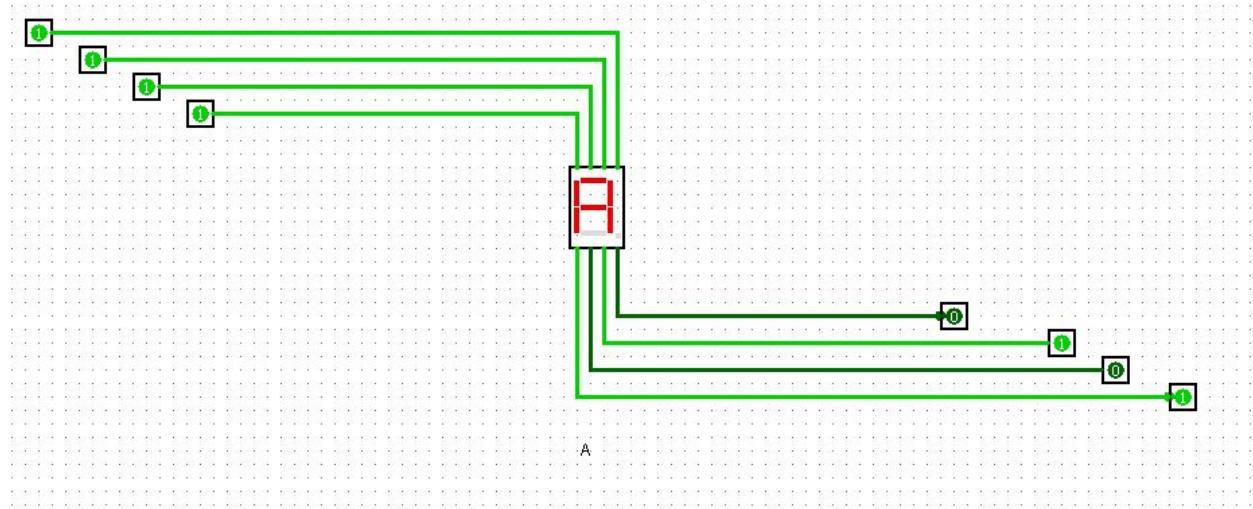


Figure B.8: A

Final output without using sequential circuit:

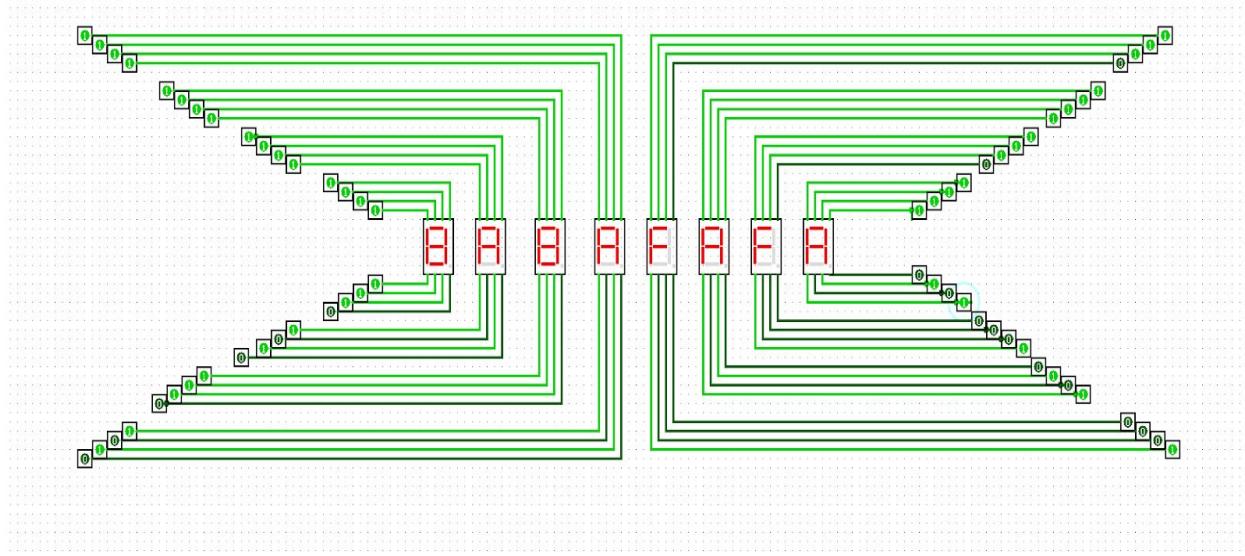


Figure B.9: Final Output

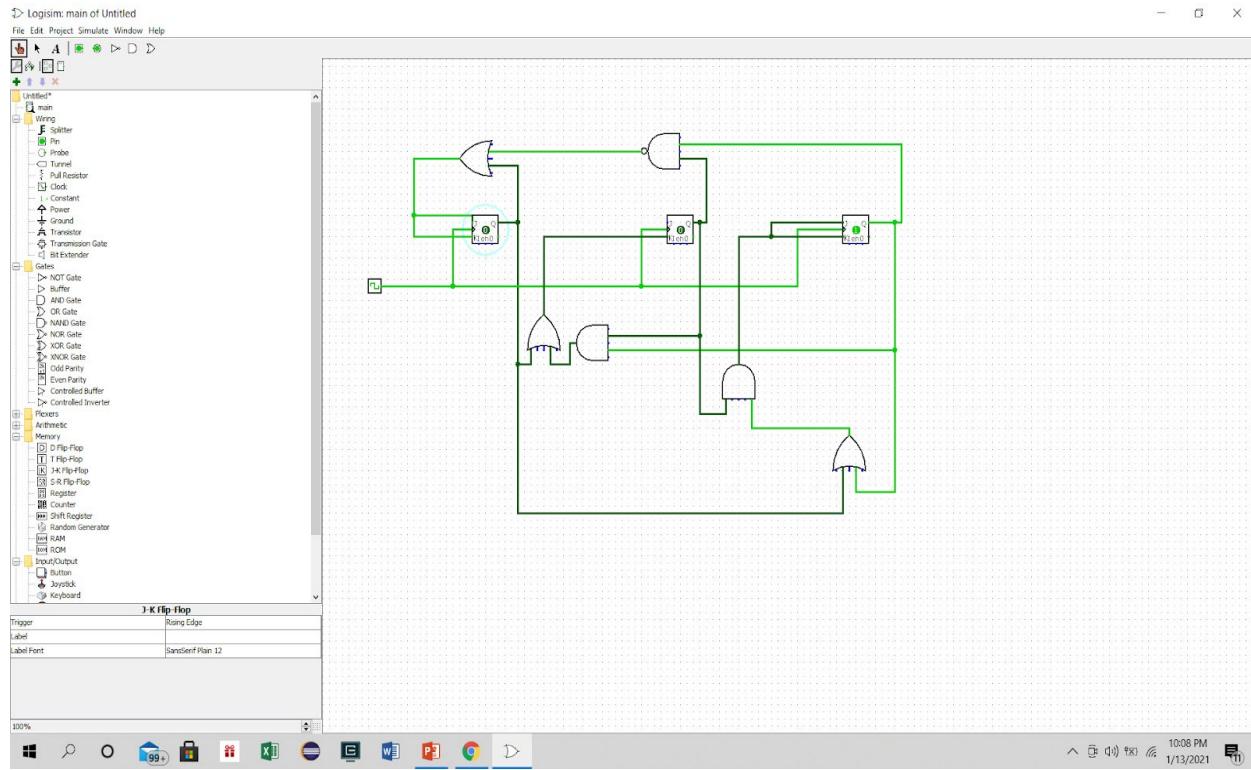


Figure B.10: Sequential Circuit

Logisim Using Sequential Circuit:

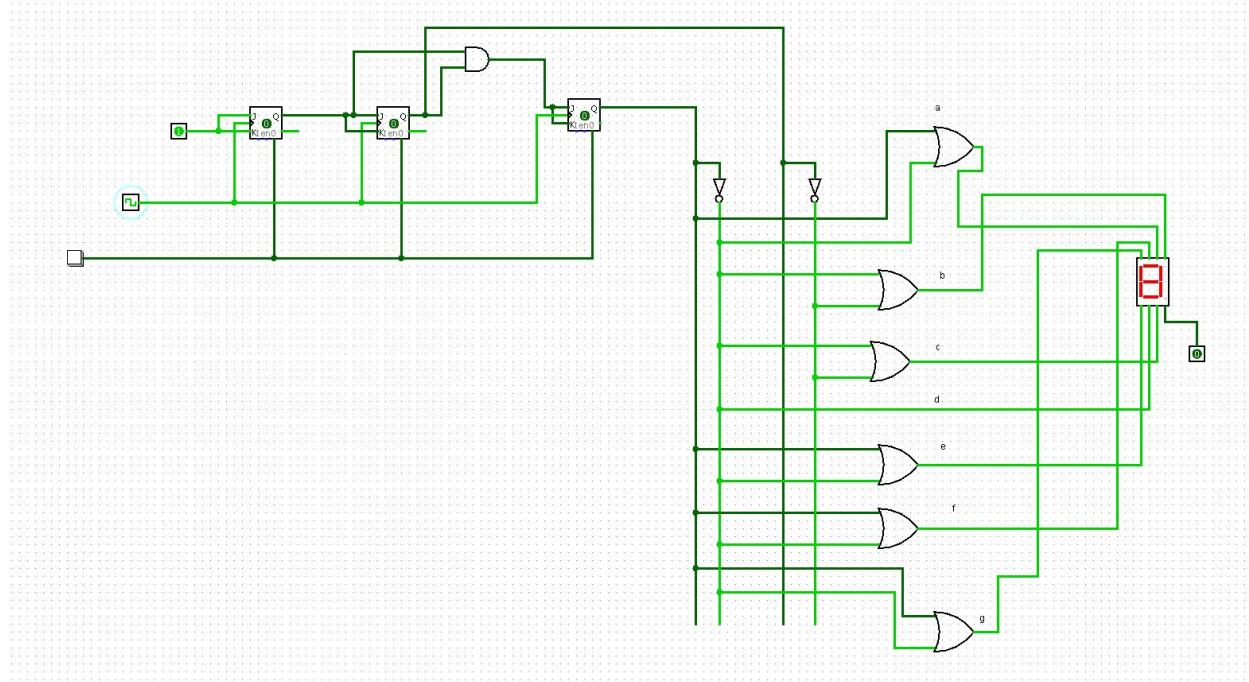


Figure B.11: B with Sequential circuit

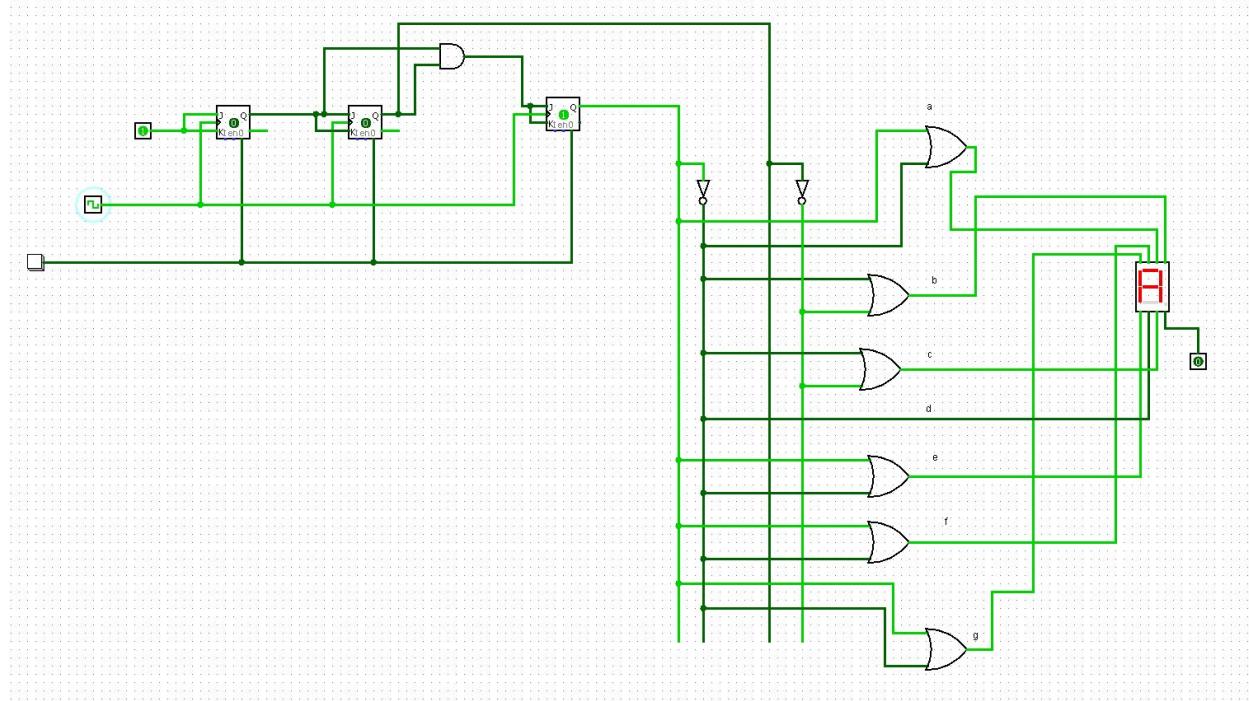


Figure B.12: A with Sequential Circuit

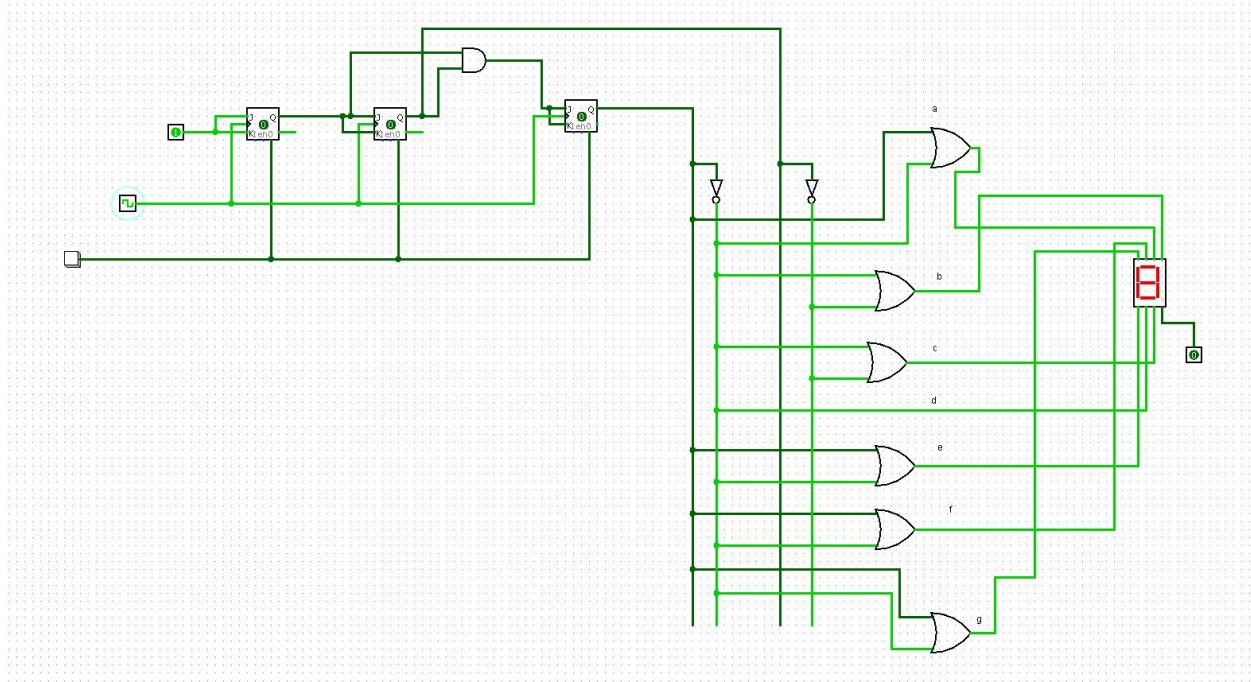


Figure B.13: B with Sequential circuit

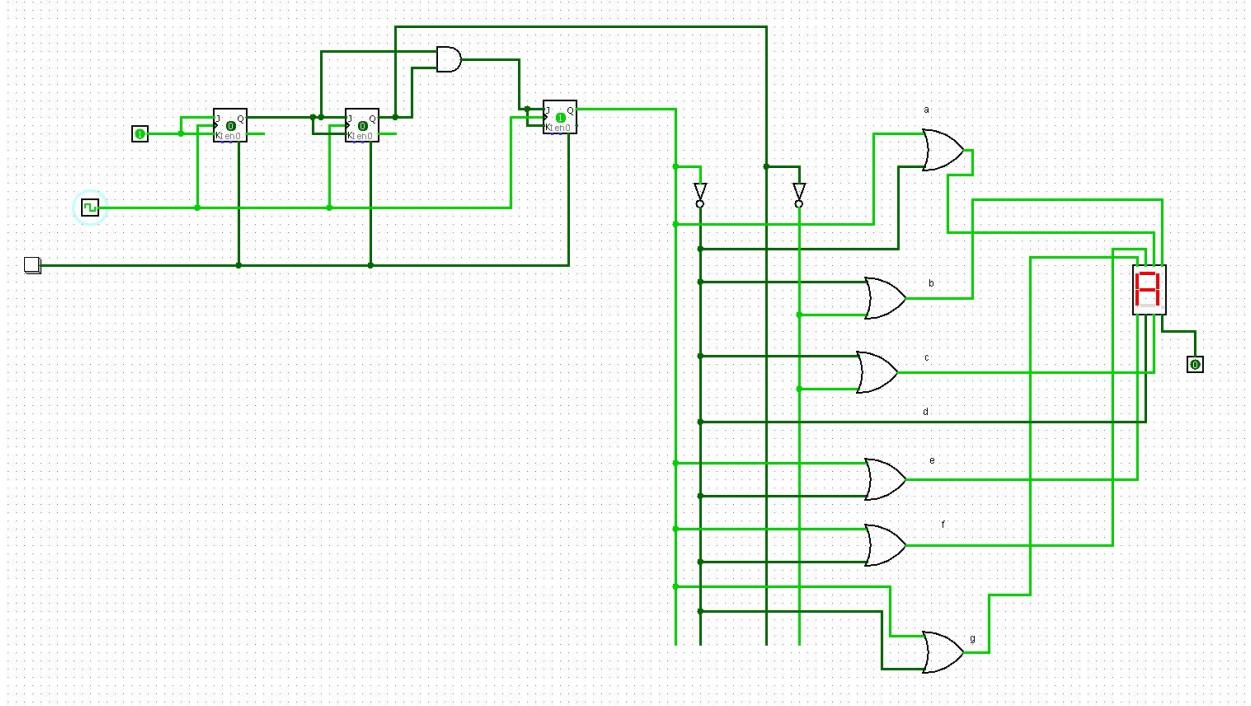


Figure B.14: A with Sequential Circuit

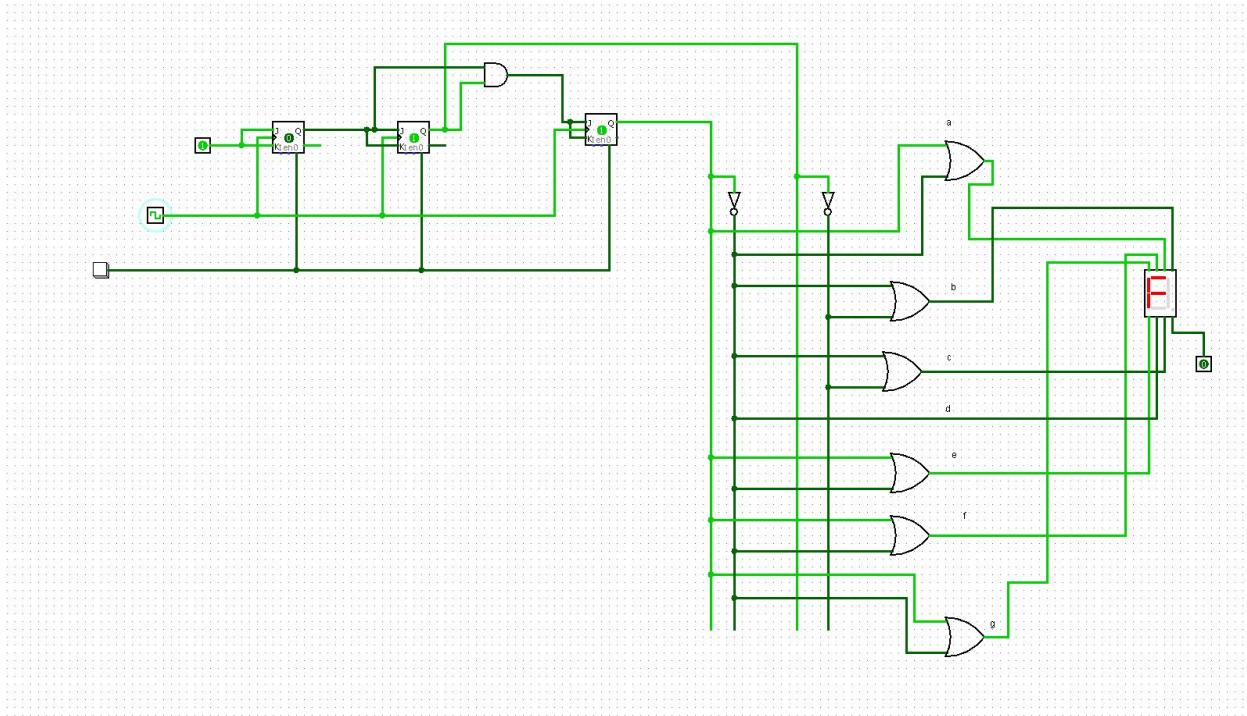


Figure B.15: F with sequential circuit

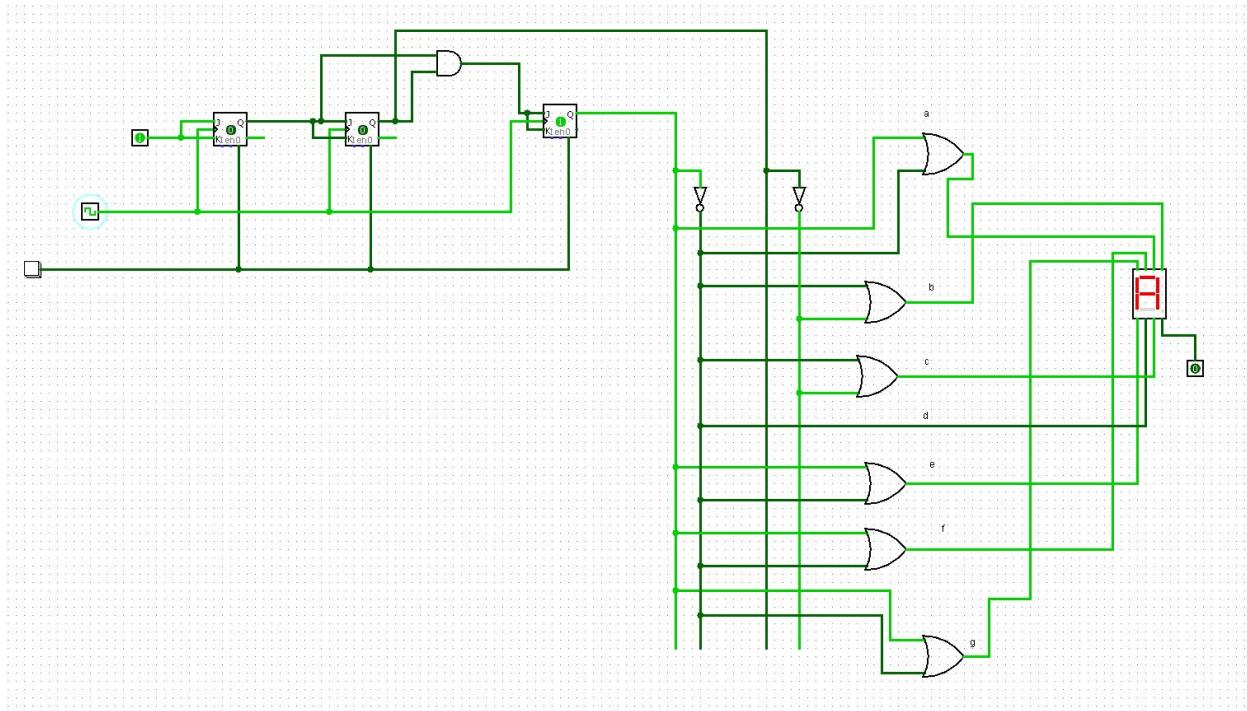


Figure B.16: A with Sequential Circuit

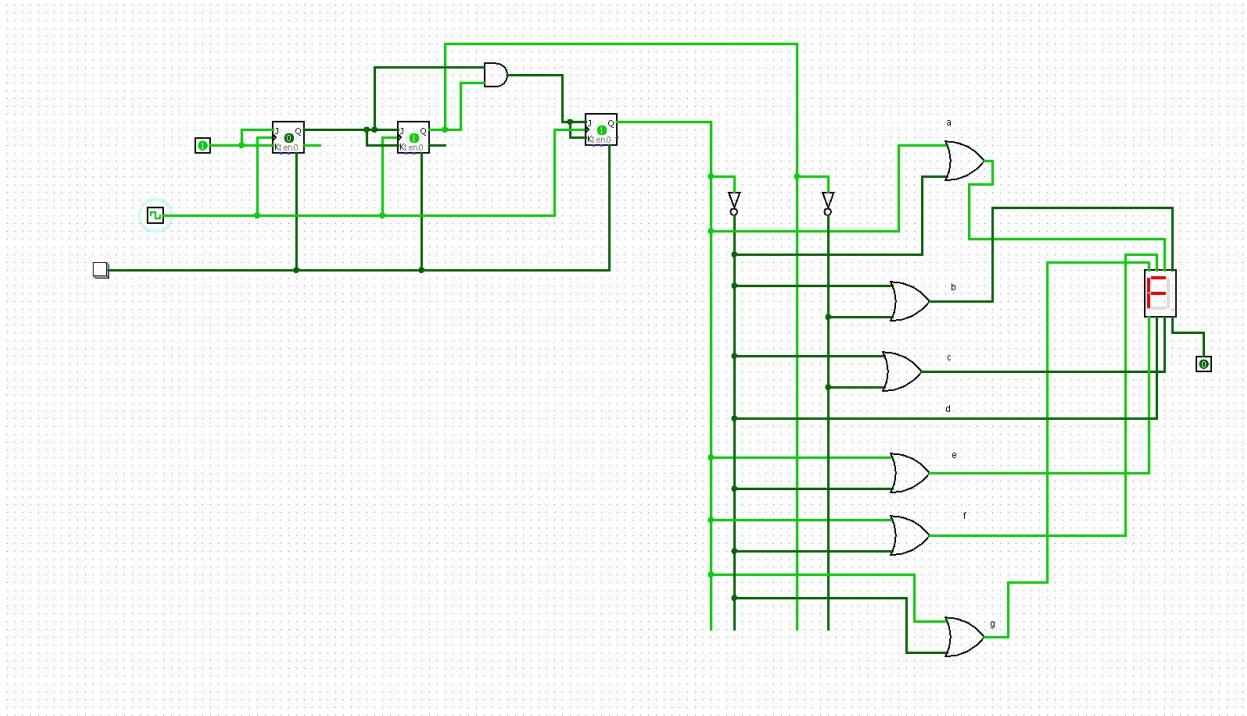


Figure B.17: F with sequential circuit

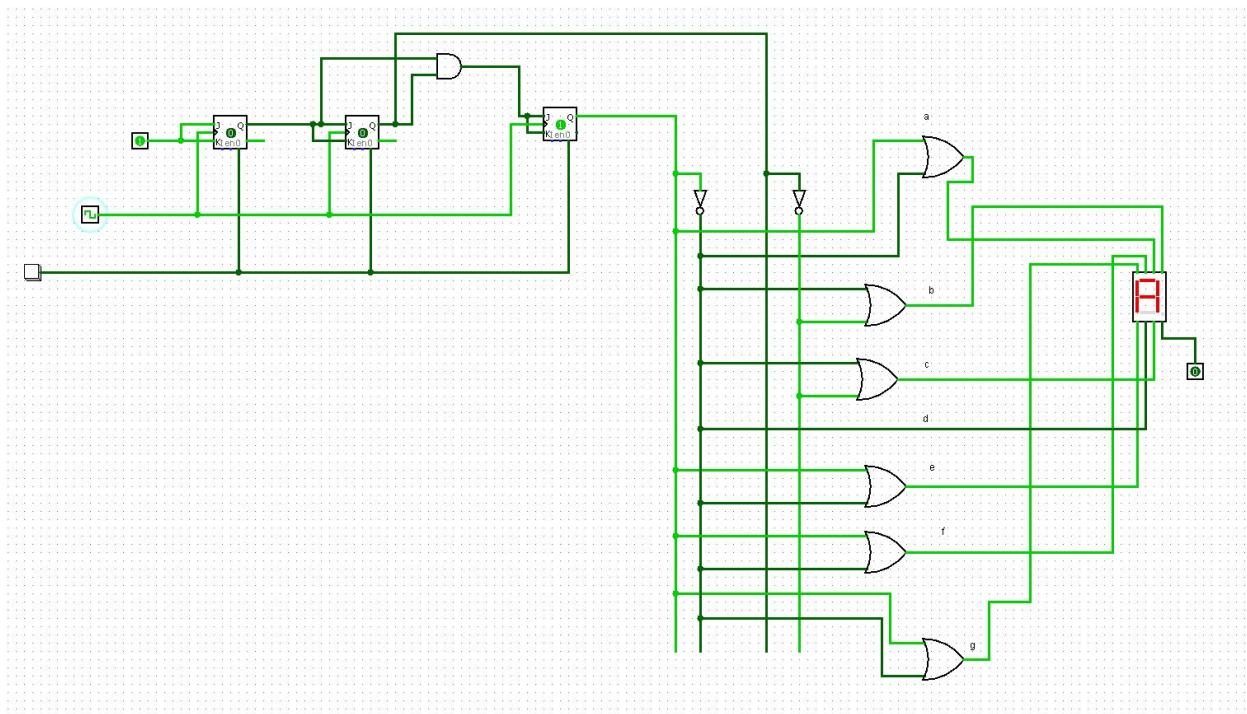


Figure B.18: A with Sequential Circuit

Conclusion:

We learn from this project, seven-segment display works by glowing the required respective LEDs in the numeral. The display is controlled using pins that are left freely. Forward biasing of these pins in a sequence will display the particular numeral or alphabet. Depending on the type of seven-segment the segment pins are applied with logic high or logic zero and in the similar way to the common pin also. We can use seven-segment display for various kinds of work.

From the truth table we got a huge equation and that could lead us to a complicated circuit. By using K-map we could minimize the equation and that will make a circuit more efficient. And we can see the outcome by using Logism.

we also learned that how sequential circuit makes things easy. And also necessity of 555 timer. Using sequential circuit we are able to use seven-segment display easily.