

ASSIGNMENT-06

Name : Monsoor Mofiz Asmani

ID : 1921079642

Course : CSE231

Section : 10.

Submitted to : Dr. Mohammad Moniruzzaman Khan

Date : 29-03-2021

Digital Logic Design

"Don't care" condition:

use of "don't care" conditions to simplify an expression.

Inputs				Output
A	B	C	D	Y
0	0	0	0	X
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	0
0	1	1	1	1
1	0	0	0	1
1	0	0	1	1
1	0	1	0	X
1	0	1	1	X
1	1	0	0	X
1	1	0	1	X
1	1	1	0	X
1	1	1	1	X

AB/CD		00	01	11	10
00	X				
01			1		
11	X	X	X	X	
10	1	1	X	X	


without don't cares:

$$Y = A\bar{B}\bar{C} + \bar{A}BCD$$

with don't cares:



$$Y = A + BCD$$

Combinational Logic Circuit:

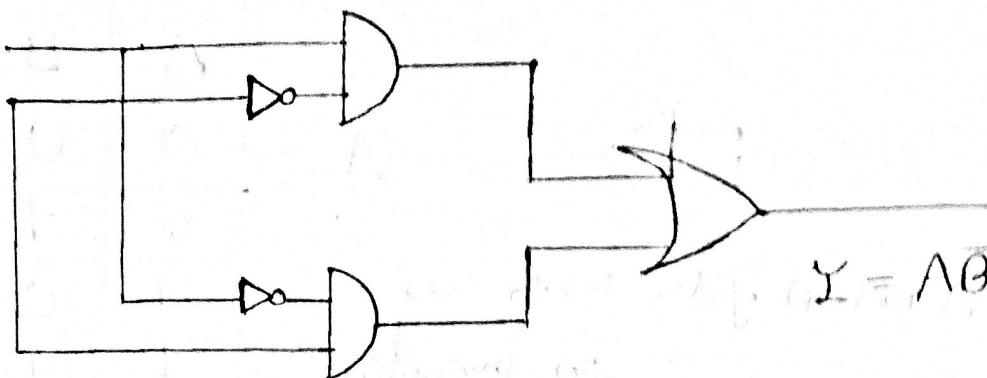


A	B	Y
0	0	0
0	1	1
1	0	1
1	1	0

$$\therefore Y = A \oplus B.$$

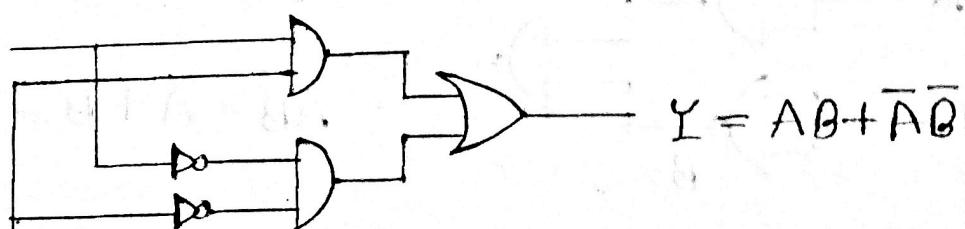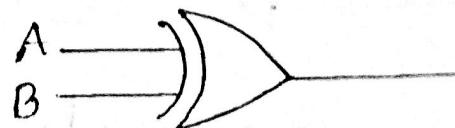

A	B	Y
0	0	1
0	1	0
1	0	0
1	1	1

$$\therefore Y = \overline{A \oplus B}$$

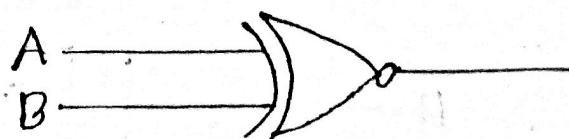

The universal property of NAND and NOR gates.

Truth table for 2 input NAND gate.

(a)



A	B	X
0	0	1
0	1	1
1	0	1
1	1	0

fig: A NAND gate used as an inverter.

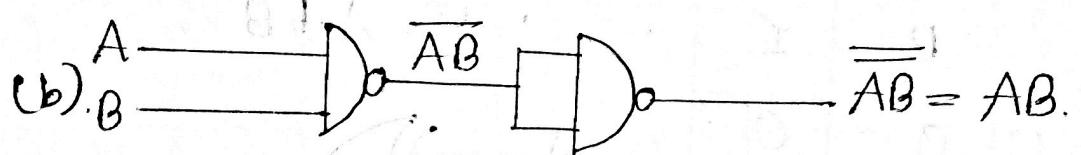


fig: Two NAND gates used as an AND gate.

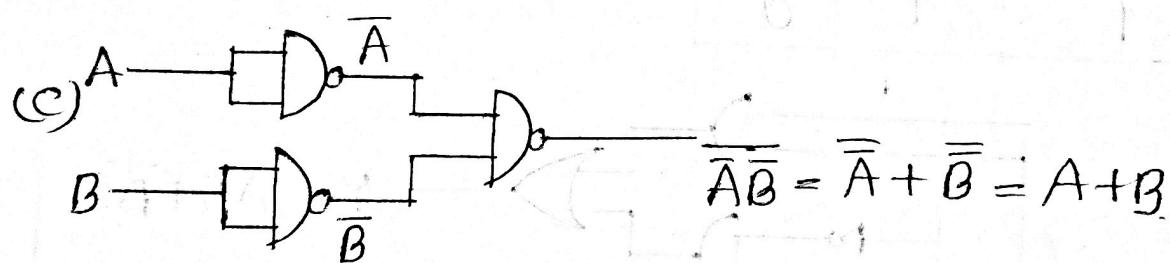


fig: Three NAND gates used as an OR gate.

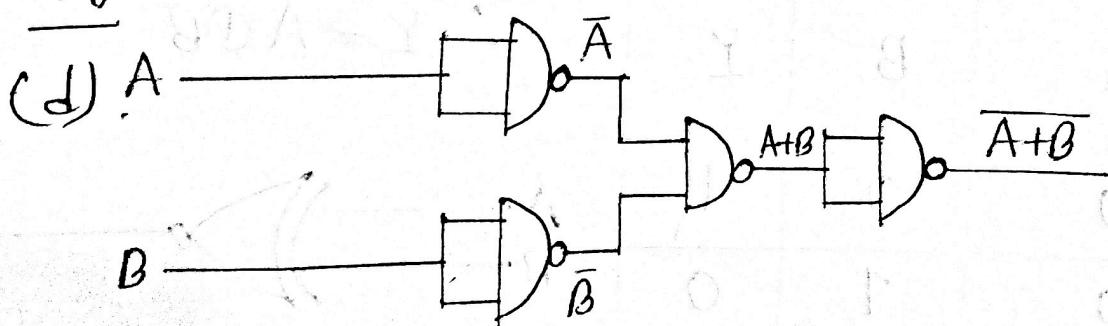


fig: Four NAND gates used as NOR gate.

The NOR Gate as a universal logic element.

Truth table for 2 input NOR Gate.


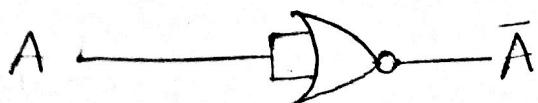


Fig: a NOR gate used as
an inverter.

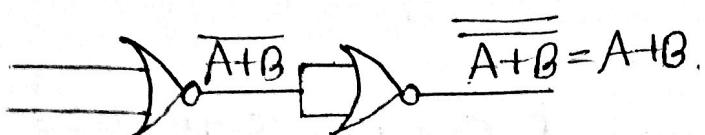

A	B	X
0	0	1
0	1	0
1	0	0
1	1	0

Fig: Two NOR gates used as an OR gate.

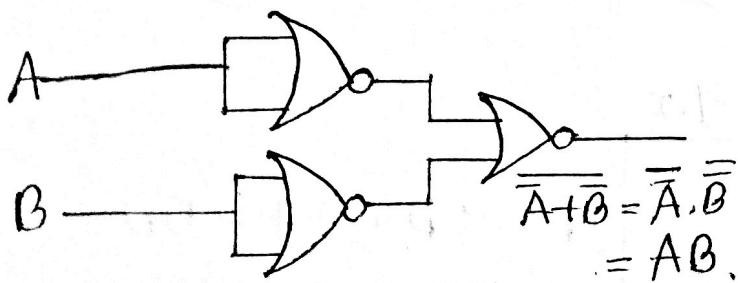


Fig: Three NOR gates used as
an AND gate.

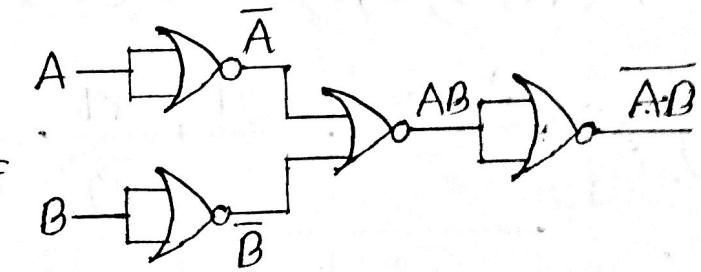


Fig: Four NOR gates used
as a NAND gate

Simplify the Boolean Function in :

- (a) Sum of products and
- (b) Product of sum form.

$$F(A, B, C, D) = \sum(0, 1, 2, 5, 8, 9, 10)$$

(a) AB \ CD

		00	01	11	10
		00	01	11	10
B		01	11	11	11
01	11	11	11	11	11
11	12	13	15	14	11
10	11	11	11	11	11

$F = \overline{BC} + \overline{BD} + \overline{ACD}$

In product of maxterms, F can be expressed as

$$F(A, B, C, D) = \prod (3, 4, 5, 7, 11, 12, 13, 14, 15)$$

(b) AB \ CD

		00	01	11	10
		00	01	11	10
B		01	01	01	01
01	01	01	01	01	01
11	01	01	01	01	01
10			01		

$F = \overline{CD} + AB + BD$

$F = \overline{CD} + AB + BD$

$= (\overline{CD}) \cdot (AB) \cdot (BD)$

$= (\overline{C} + \overline{D}) (A+B) (B+D)$

Combinational Logic using NAND and NOR gates:

NAND gate:

using De Morgan's rule :

$$\overline{AB} = \overbrace{\overline{A} + \overline{B}}$$

Negative OR.


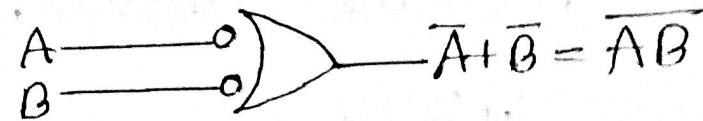
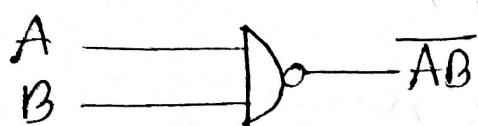


Fig : Two graphic symbols for NAND gate.

$$\overline{A+B} + \overline{AB}$$

Negative AND.

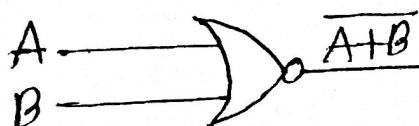

OR-invert.

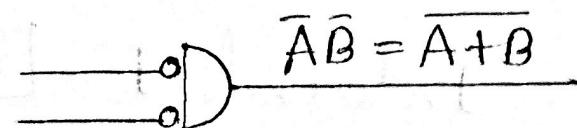


Fig : Two graphic symbols for NOR gate.

Exercise 01 :

$$F(w, x, y, z) = \Sigma(1, 3, 7, 11, 15)$$

$$d(w, x, y, z) = \Sigma(0, 2, 5) \quad \underbrace{y}_{z}$$

w\yz	00	01	11	10
00	X	1	1	X
01	0	X	1	0
11	0	0	1	0
10	0	0	1	0

$$F = \bar{w}z + yz \quad (\text{Combining } 10z \text{ and } x's)$$

w\yz	00	01	11	10
00	X	1	1	X
01	0	X	1	0
11	0	0	1	0
10	0	0	1	0

$$\bar{F} = \bar{y}\bar{z} + w\bar{y} + y\bar{z}$$

$$= \bar{z}(\bar{y}+y) + w\bar{y}$$

$$= \bar{z} \cdot 1 + w\bar{y} \quad [\because \bar{y}+y=1]$$

$$= \bar{z} + w\bar{y}$$

$$\therefore F = \overline{\bar{z} + w\bar{y}}$$

$$= \bar{z} \cdot (\bar{w}\bar{y})$$

$$= z(\bar{w}+y). \text{(Combining } 0's \text{ and } x's).$$

Exercise 02 :

$$F(A, B, C, D) = \sum (5, 7, 8, 10, 11, 14, 15)$$

$$d = \sum (0, 12, 13)$$

		AB	CD	00	01	10	11	C
		00		X	0	0	0	0
		01		0	1	1	1	0
A	11	12	X	13	X	15	1	1
	10	8	1	9	0	11	1	1

$$\therefore F = A\bar{D} + BD + AC^D$$

$$= BD + A(C + \bar{D})$$

		CD		00		01		11		10		C
		A	B	00	01	11	10					
A	00	0	1	X	0	0	0	0	0	0	0	
	01	1	0	0	1	1	1	1	1	0	0	
	11	1	1	X	1	1	1	1	1	1	1	
	10	1	0	1	0	1	1	1	1	1	1	D

$$\bar{F}_d = \bar{A}\bar{D} + \bar{A}\bar{B} + A\bar{C}D.$$

$$= \bar{A}(\bar{B} + \bar{D}) + A\bar{C}D.$$

$$\therefore F_d = \bar{A}(\bar{B} + \bar{D}) + A\bar{C}D$$

$$= \overline{\bar{A}(\bar{B} + \bar{D})} \cdot \overline{A\bar{C}D}$$

$$= (\bar{A} + \overline{\bar{B} + \bar{D}}) \cdot (\bar{A} + \bar{C} + \bar{D})$$

$$= (A + (\bar{B} \cdot \bar{D})) \cdot (\bar{A} + C + D)$$

$$= (A + BD)(\bar{A} + C + D). \quad (\text{Ans})$$

Exercise 03 :

$$F(A, B, C, D) = \sum(2, 4, 10, 12, 14)$$

$$d(A, B, C, D) = \sum(0, 1, 5, 8) \underbrace{C}_{C}$$

AB \ CD	00	01	11	10
00	X	X	O	1
01	1	X	O	O
11	1	O	O	1
10	X	O	O	1

$$F = \bar{C}\bar{D} + \bar{A}\bar{C} + A\bar{D} + \bar{B}\bar{D}$$

$$= \bar{C}(A+\bar{D}) + \bar{D}(A+\bar{B}).$$

		AB	CD	C			
		00	01	11	10		
A	0	X	X	O	1		
	1	1	X	O	O		
B	0	1	O	O	1		
	1	X	O	O	1		

$$F = \overline{BC} + \overline{CD} + CD + \overline{ABC}$$

$$= \overline{BC} + D(\overline{C}+C) + \overline{ABC}$$

$$= \overline{BC} + D \cdot 1 + \overline{ABC}$$

$$= \overline{ABC} + \overline{BC} + D.$$

$$F = \overline{\overline{ABC} + \overline{BC} + D}$$

$$= (\overline{\overline{ABC}}), (\overline{\overline{BC}}), \overline{D}$$

$$= (\overline{\overline{A}} + \overline{B} + \overline{C}), (\overline{\overline{B}} + \overline{C}), \overline{D}$$


$$= (A + B + C), (B + C), \overline{D}$$

(Ans)

Exercise 04:

$$F(A, B, C, D) = \prod(1, 3, 5, 7, 13, 15).$$

$$d(A, B, C, D) = \prod(8, 12, 14).$$

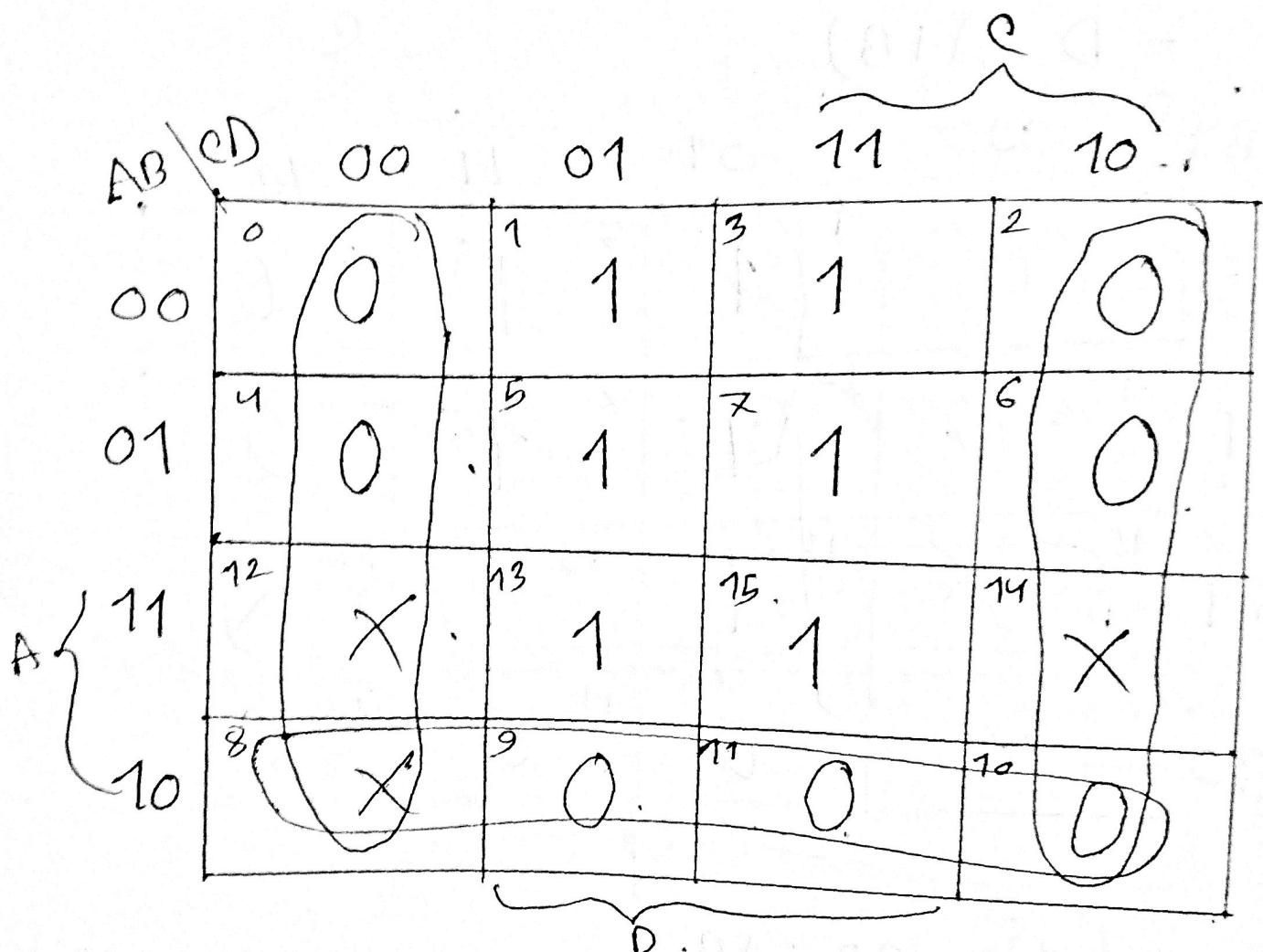

$$\overline{F} = \overline{C}\overline{D} + C\overline{D} + A\overline{B}.$$

$$= \overline{D}(\overline{C}+C) + A\overline{B}$$

$$= \overline{D} \cdot 1 + A\overline{B} \quad [\because \overline{C}+C=1]$$

$$= \overline{D} + A\overline{B}.$$

$$\therefore F = \overline{D + AB}$$

$$= \overline{D} \cdot (\overline{AB})$$

$$= \overline{D} \cdot (\overline{A} + \overline{B})$$

$$= D (\overline{A} + B)$$

		00	01	11	10	c
		00	1	3	2	
		01	5	7	6	
A	11	12	X	13	14	
	10	8	X	9	10	
		D				

$$F = \overline{A}D + BD + AB$$

$$= AB + D(\overline{A} + B)$$

(Ans).

Exercise 05:

$$F(A, B, C, D) = \overline{P}(1, 3, 6, 9, 11, 12, 14)$$

$$d(A, B, C, D) = \overline{P}(2, 4, 10, 13, 15)$$

AB \ CD		00	01	11	10
		0	1	3	2
		4	5	7	6
A \ {	00	0	1	1	X
	01	X	0	0	1
	11	1	X	X	1
	10	0	1	1	X

$$\bar{F} = BD + \bar{B}\bar{D} \quad \therefore F = \overline{BD + \bar{B}\bar{D}} = \overline{(B+\bar{D})(\bar{B}+D)} = \overline{(B+\bar{D})} \cdot \overline{(B+D)} = \overline{B} \cdot \overline{D}$$

AB \ CD		00	01	11	10
		0	1	3	2
		4	5	7	6
A \ {	00	0	1	1	X
	01	X	0	0	1
	11	1	X	X	D
	10	0	1	1	X

$$F = BD + \bar{B}\bar{D} + C\bar{D} + AB = AB + \bar{B}\bar{D} + \bar{D}(B+C)$$